

EXPERIMENT 10 : ASYNCHRONOUS COUNTER

AIM: Implementation of asynchronous counter using flip-flop

LEARNING OBJECTIVE:

To design & implement Asynchronous counter using IC 7476

Objective is to learn about Asynchronous, Synchronous Up, Down Counter and its application.

COMPONENTS REQUIRED: IC 7476, IC 7404, LED's ,resistors(180 ohms)

PROBLEM STATEMENT:


Design a 3 bit asynchronous counter using IC 7476.

THEORY:

Counters are the sequential circuits which change the state in particular sequence. They have cyclic state diagram..these circuits can be realized using JK or T flipflop.

In Asynchronous counter, all the flipflops are not triggered by common system clock but transition in one flipflop state triggers the next flipflop and with n number of flipflop counter can give upto 2^n number of states

3- Bit Asynchronous Counter.

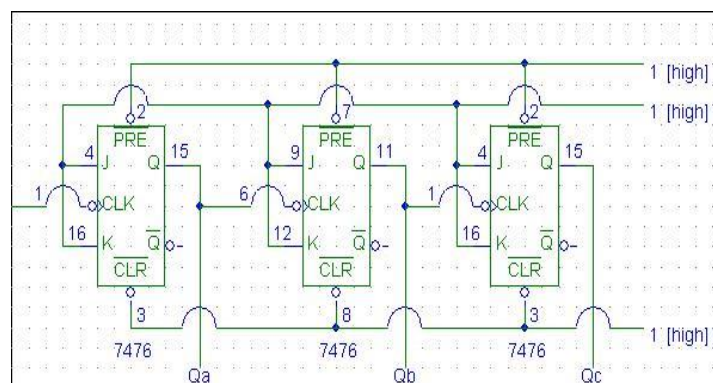

Experimental Procedure

1. Make the connections as per the logic diagram.
2. Observe the output of the circuit.

POST LAB QUESTIONS:

- 1.What is an asynchronous counter?
- 2.How is it different from a synchronous counter?
- 3.Explain glitch problem in Asynchronous counter.

Post