

EXPERIMENT: 7 COMPARATORS

AIM: To realize One & Two Bit Comparator and study of 7485 magnitude comparator.

LEARNING OBJECTIVE:

- To learn about various applications of comparator
- To learn and understand the working of IC 7485 magnitude comparator
- To learn to realize 8-bit comparator using 4-bit comparator

THEORY:

Magnitude Comparator is a logical circuit, which compares two signals A and B and generates three logical outputs, whether $A > B$, $A = B$, or $A < B$. IC 7485 is a high speed 4-bit Magnitude comparator, which compares two 4-bit words. The $A = B$ Input must be held high for proper compare operation.

COMPONENTS REQUIRED:

IC 7400, IC 7410, IC 7420, IC 7432, IC 7486, IC 7402, IC 7408, IC 7404, IC 7485, Patch Cords


1) 1- BIT COMPARATOR

TRUTH TABLE

$$A > B = A \bar{B}$$

$$A < B = \bar{A} B$$

$$A = B = \bar{A} \bar{B} + AB$$

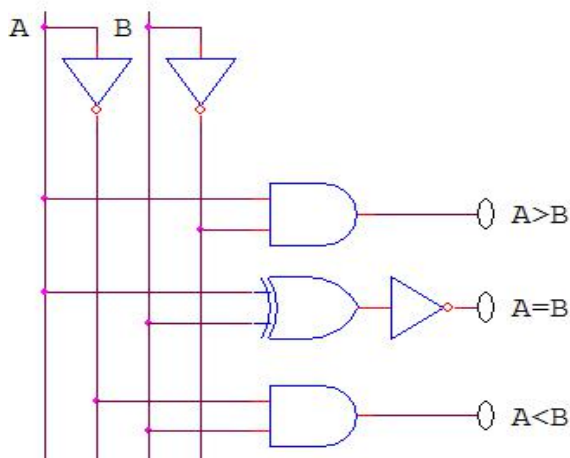


INPUTS		OUTPUTS		
A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

2) 2- BIT COMPARATOR

$$(A > B) = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + \bar{B}_0 A_1 A_0$$

$$(A = B) = (A_0 \bar{B}_0) (A_1 \bar{B}_1)$$

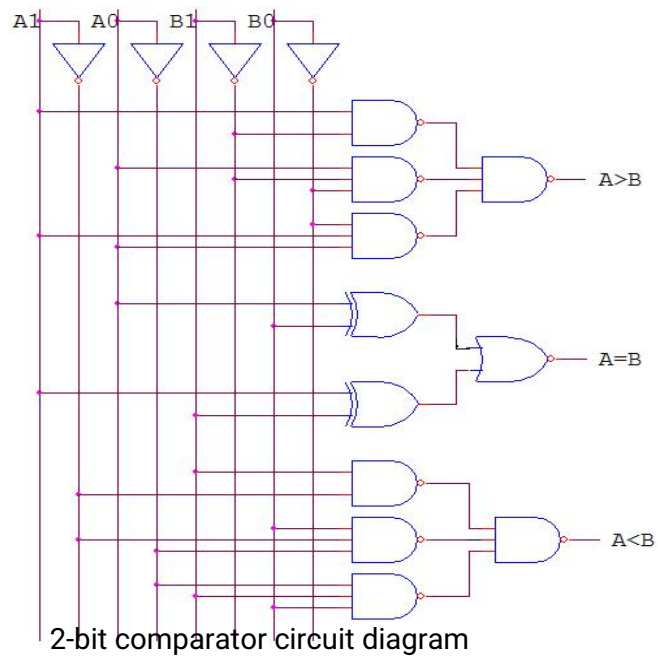
$$(A < B) = B_1 A_1 + B_0 A_1 A_0 + A_0 B_1 B_0$$



TRUTH TABLE

INPUTS				OUTPUTS		
A1	A0	B1	B0	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

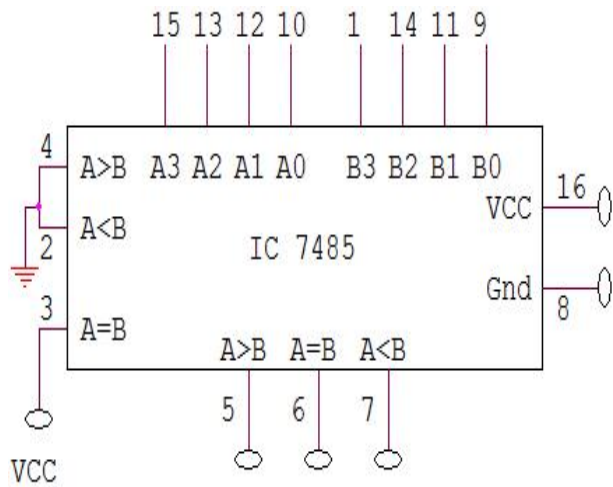3) TO COMPARE THE GIVEN DATA USING 7485 CHIP.



A				B				Result
A3	A2	A1	A0	B3	B2	B1	B0	
0	0	0	1	0	0	0	0	A > B
0	0	0	1	0	0	0	1	A = B
0	0	0	0	0	0	0	1	A < B

PROCEDURE:

- 1 Check all the components for their working.
- 2 Insert the appropriate IC into the IC base.
- 3 Make connections as shown in the circuit diagram.
- 4 Verify the Truth Table and observe the outputs.

Postlab Questions

1. Design 8 bit comparator using two 7485
2. Write applications of Comparator