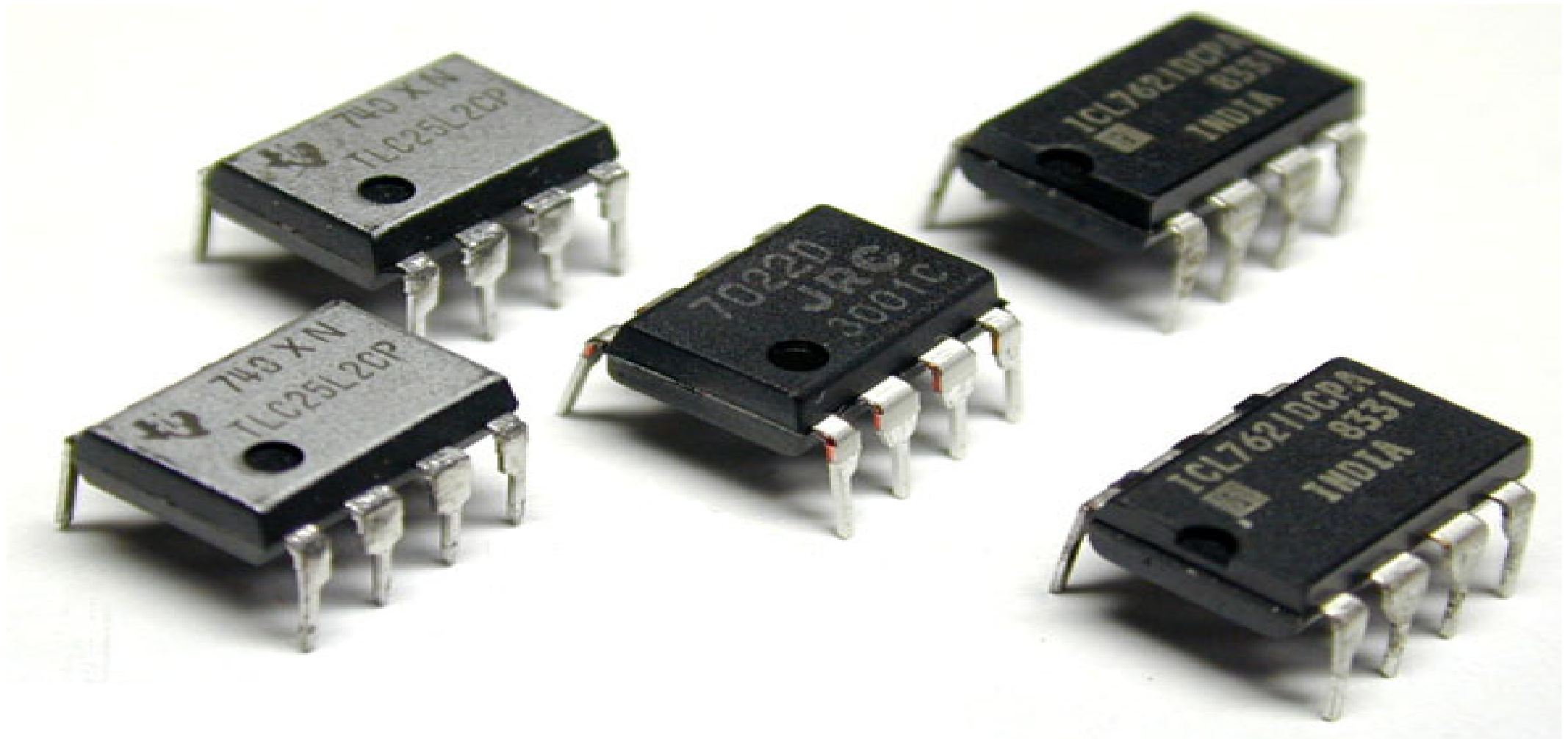


# Operational Amplifier (Op – Amp)


## Component Description

---




# Operational Amplifier (Op – Amp)
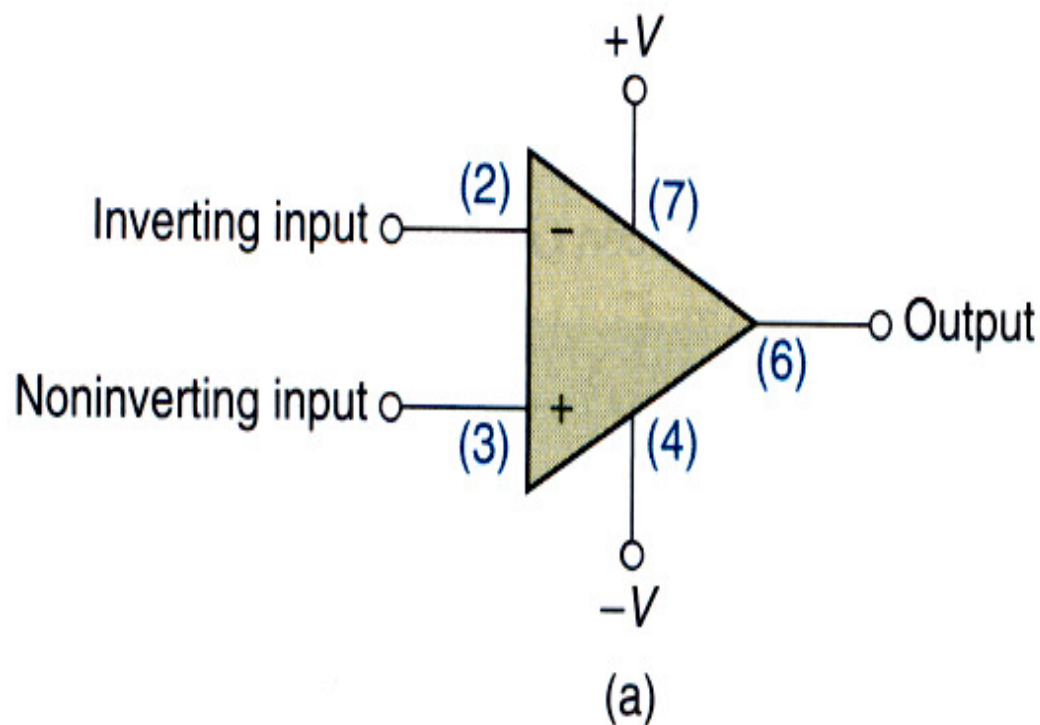
## Pin Diagram & Circuit Symbol of IC 741




(b) The schematic symbol for an op-amp

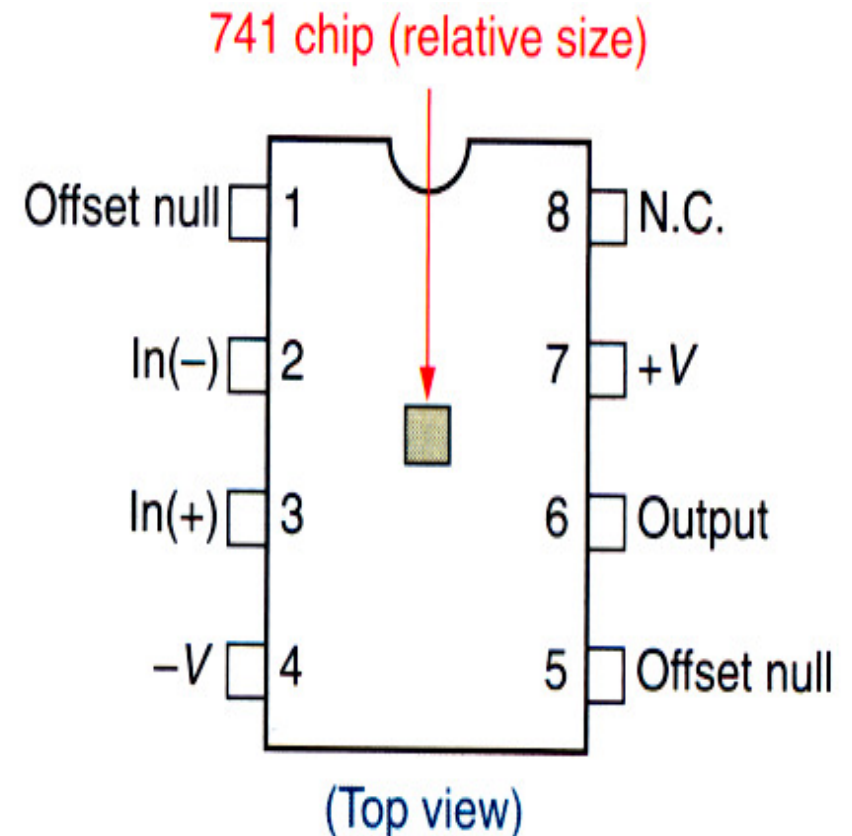


(c) The 741 chip packaged in an 8-pin DIP (dual-in-line package)

# Operational Amplifier (Op – Amp)

## Types of Op – Amp Packages of IC 741

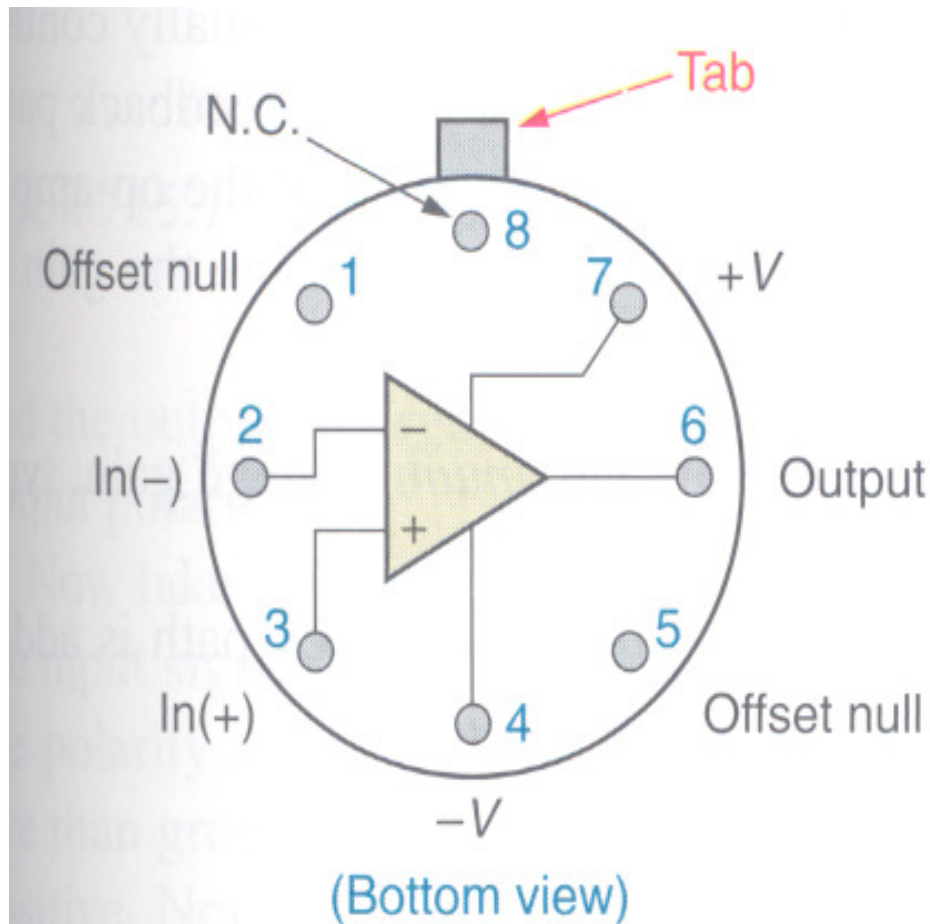


(a) Metal can (TO-5)

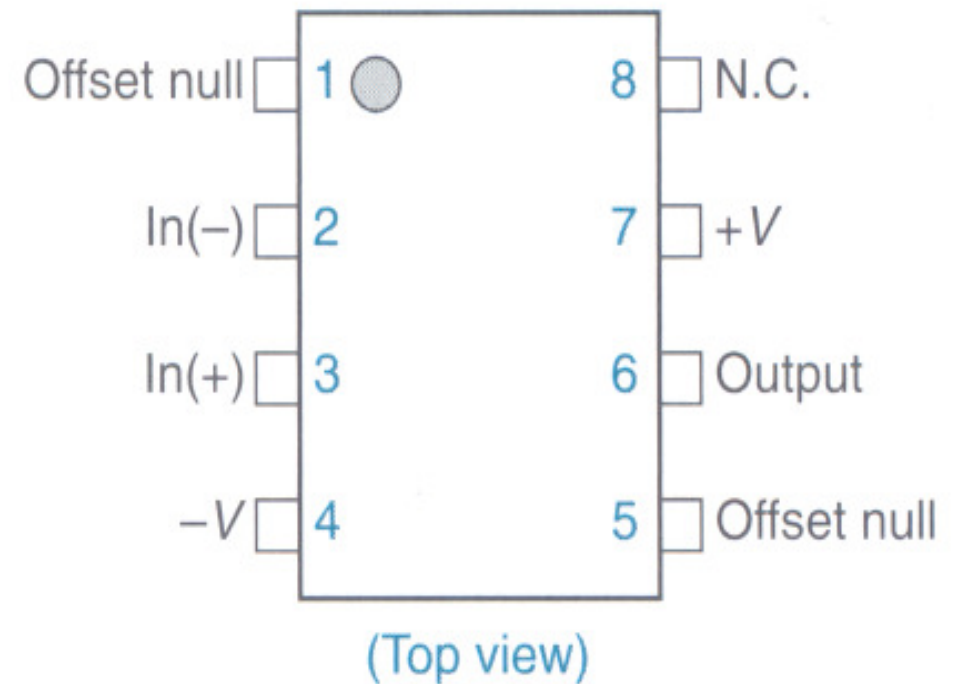

(b) 8-pin DIP or SMP

# Operational Amplifier (Op – Amp)

## What makes it so useful & versatile ?

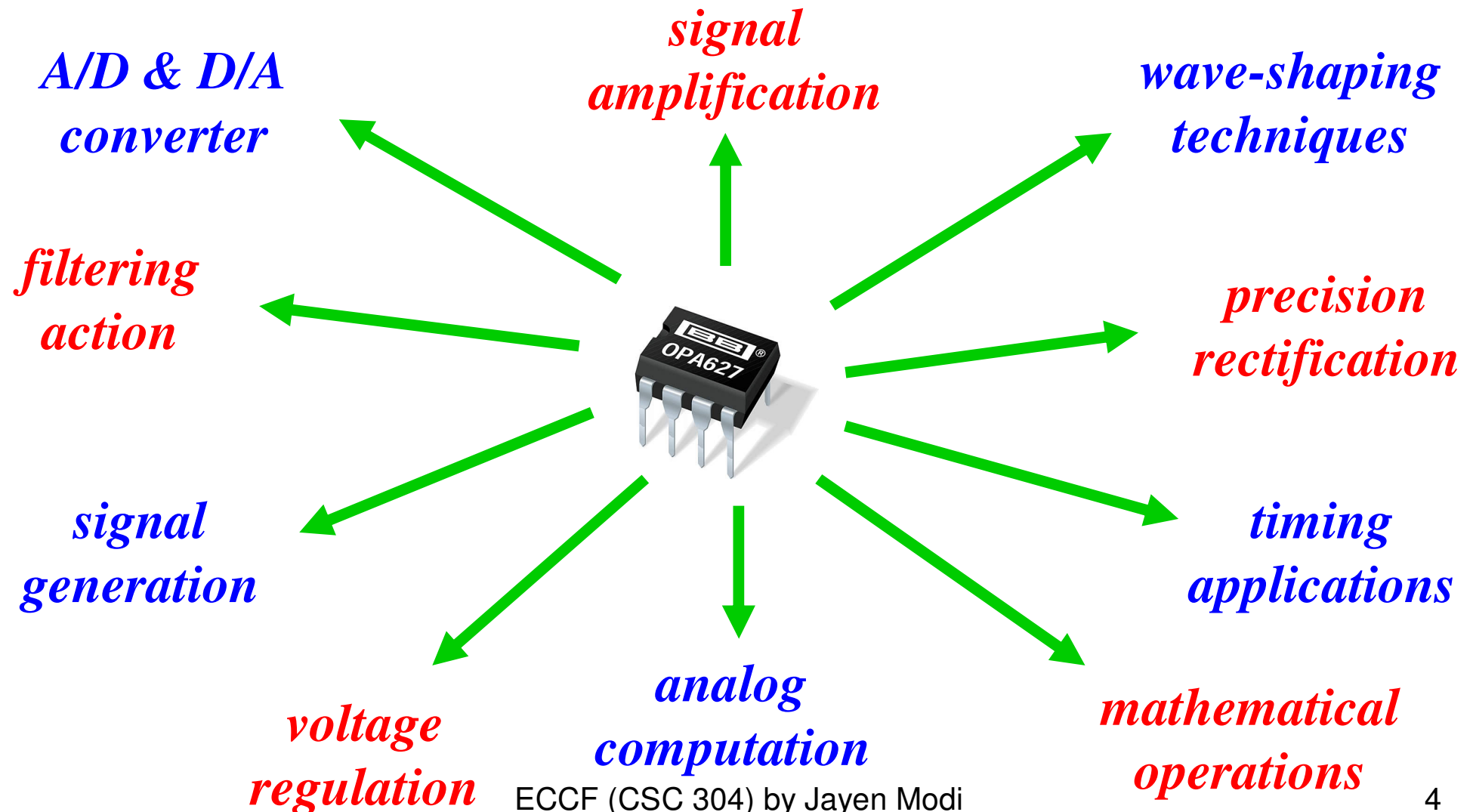

---

# **Operational Amplifier (Op – Amp)**


## **Typical Application Areas**

---

- **Analog & Digital Communication**
- **Instrumentation Systems**
- **Analog Signal Processing**
- **Analog Computation Systems**
- **Waveform Synthesizers & Generators**
- **Signal Conversion Techniques**
- **Voltage Regulators & Power Supplies**
- **Timers & Timing Applications**

# Operational Amplifier (Op – Amp)

## Circuit Symbol of IC 741C

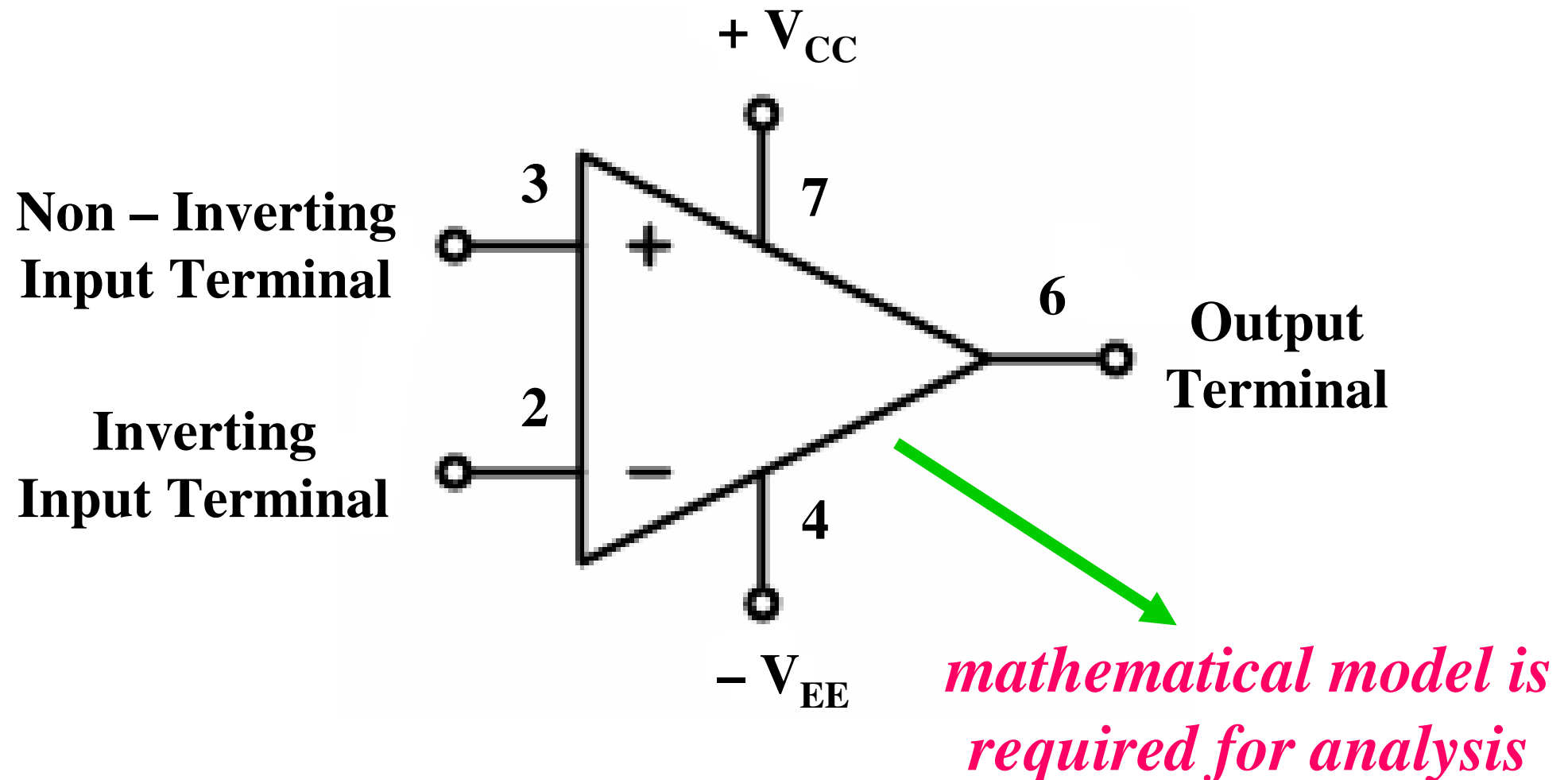

---

# Concept of Mathematical Models

## Electrical Equivalent Circuit

---


*A mathematical model is the combination of circuit elements, properly chosen, that best approximates the actual behaviour of a semiconductor device under some certain specific operating conditions.*



*Remember Thevenin's Theorem ?*

# Operational Amplifier (Op – Amp)


## Ideal Mathematical Model

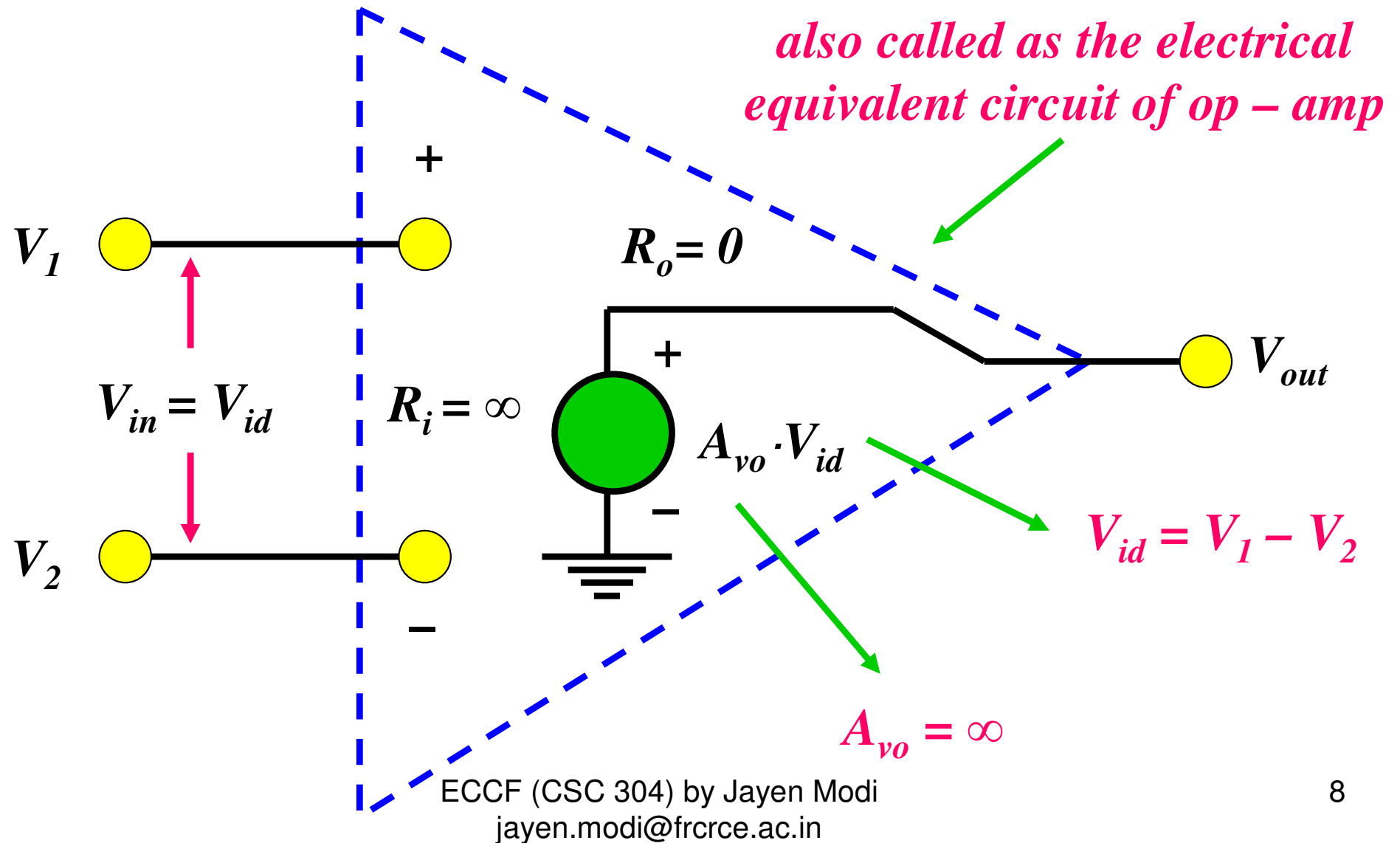




# Ideal Operational Amplifier

## Open Loop Transfer Characteristics

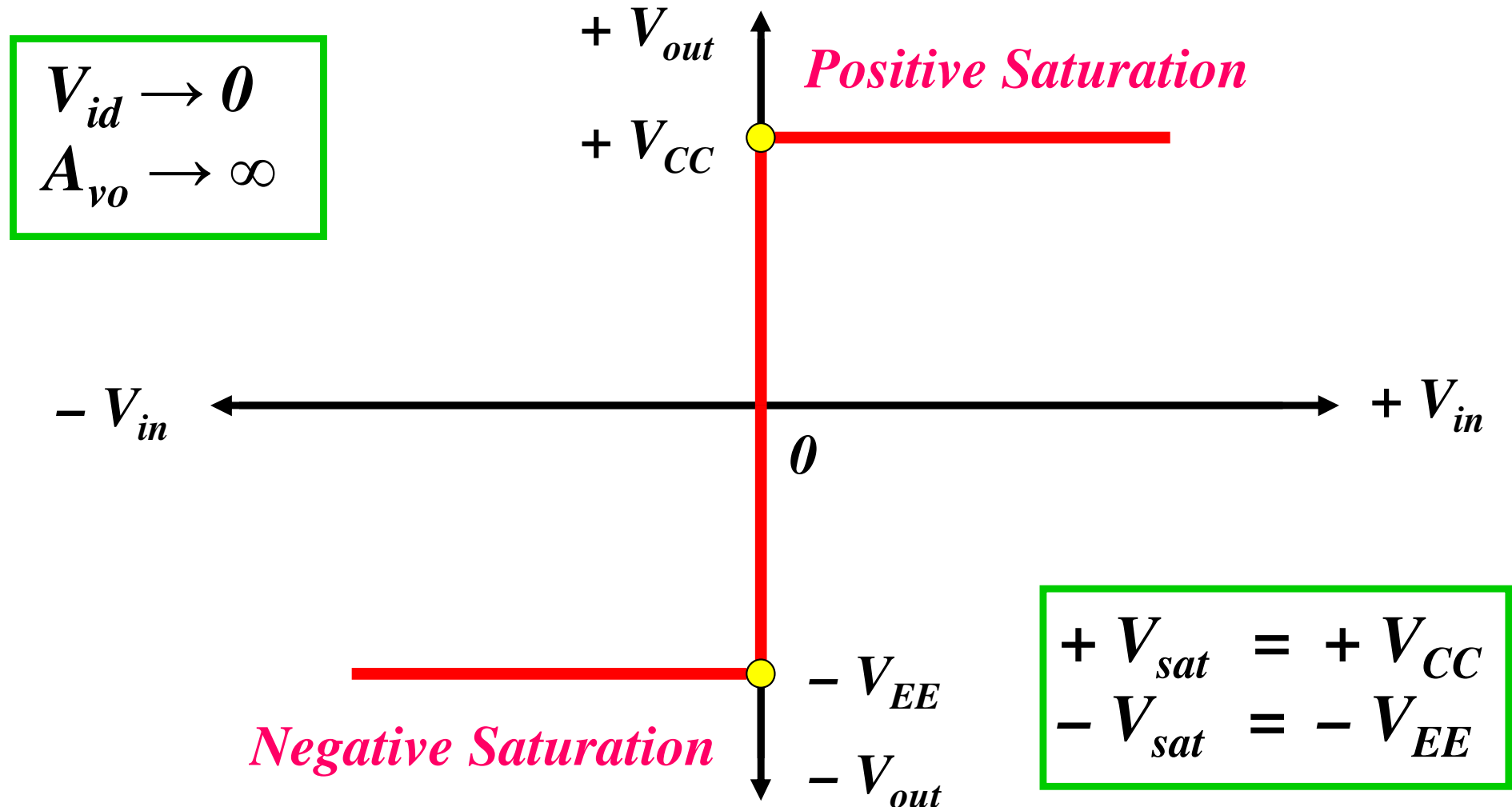


# Operational Amplifier (Op – Amp)

## Practical Mathematical Model

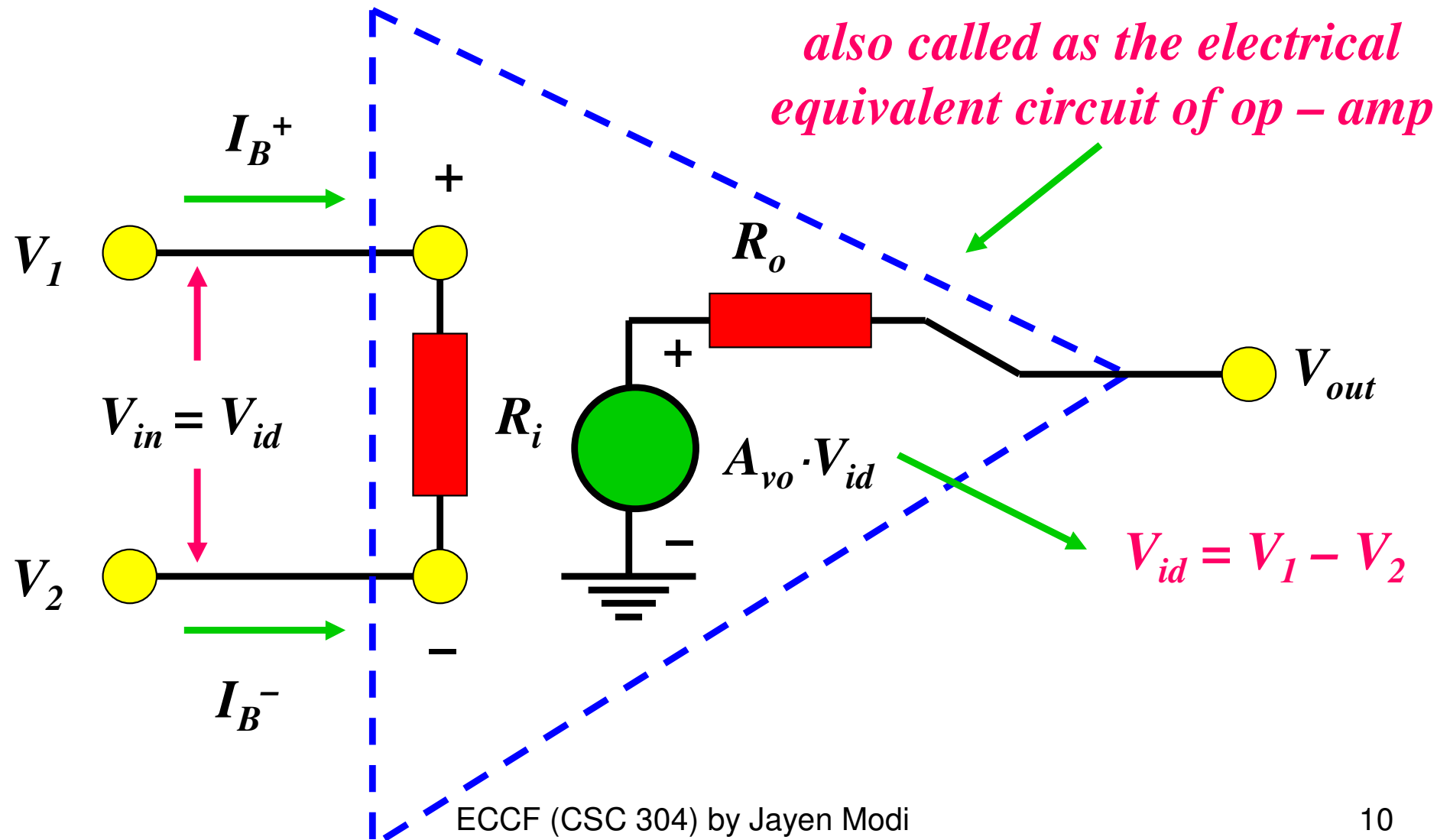

# Practical Operational Amplifier

## Open Loop Transfer Characteristics

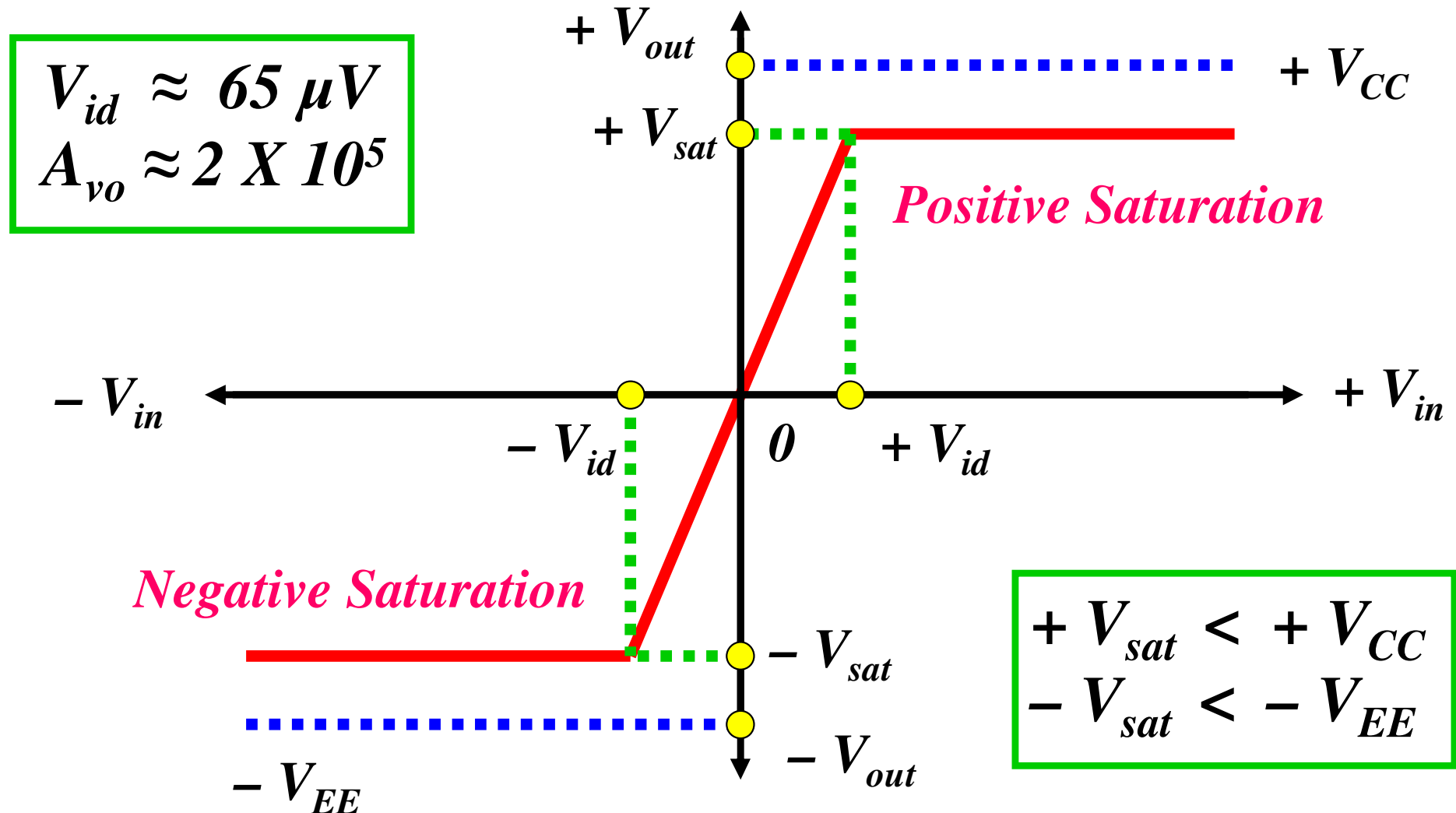

# Practical Operational Amplifier

## Types of 'Working' Configurations

- **Open Loop Configuration**

- **Difference Amplifier**

- **Inverting Amplifier**


- **Non – Inverting Amplifier**

*never used in actual practice  
for linear applications . . .  
... but used as comparator*

- **Closed Loop Configuration**

- **Wide variety of applications**

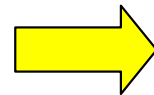*All are linear applications  
but with 'reduced' gain*




*Inverting Amplifier  
Non – Inverting Amplifier  
Summing Amplifier  
Averaging Amplifier  
Adder & Subtractor  
Integrator & Differentiator*

# Practical Operational Amplifier
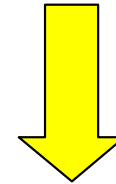
## Applications in Open Loop Configuration

- Difference Amplifier
- Inverting Amplifier
- Non – Inverting Amplifier


*never used in actual practice  
for linear applications . . .  
. . . but used as comparator*



*That's because in open loop configuration as gain approaches infinity, a small change in the input voltage ( $V_{id}$ ) will cause the output of op-amp to go either at  $+V_{sat}$  or  $-V_{sat}$  making it useless for linear applications*


# Practical Operational Amplifier
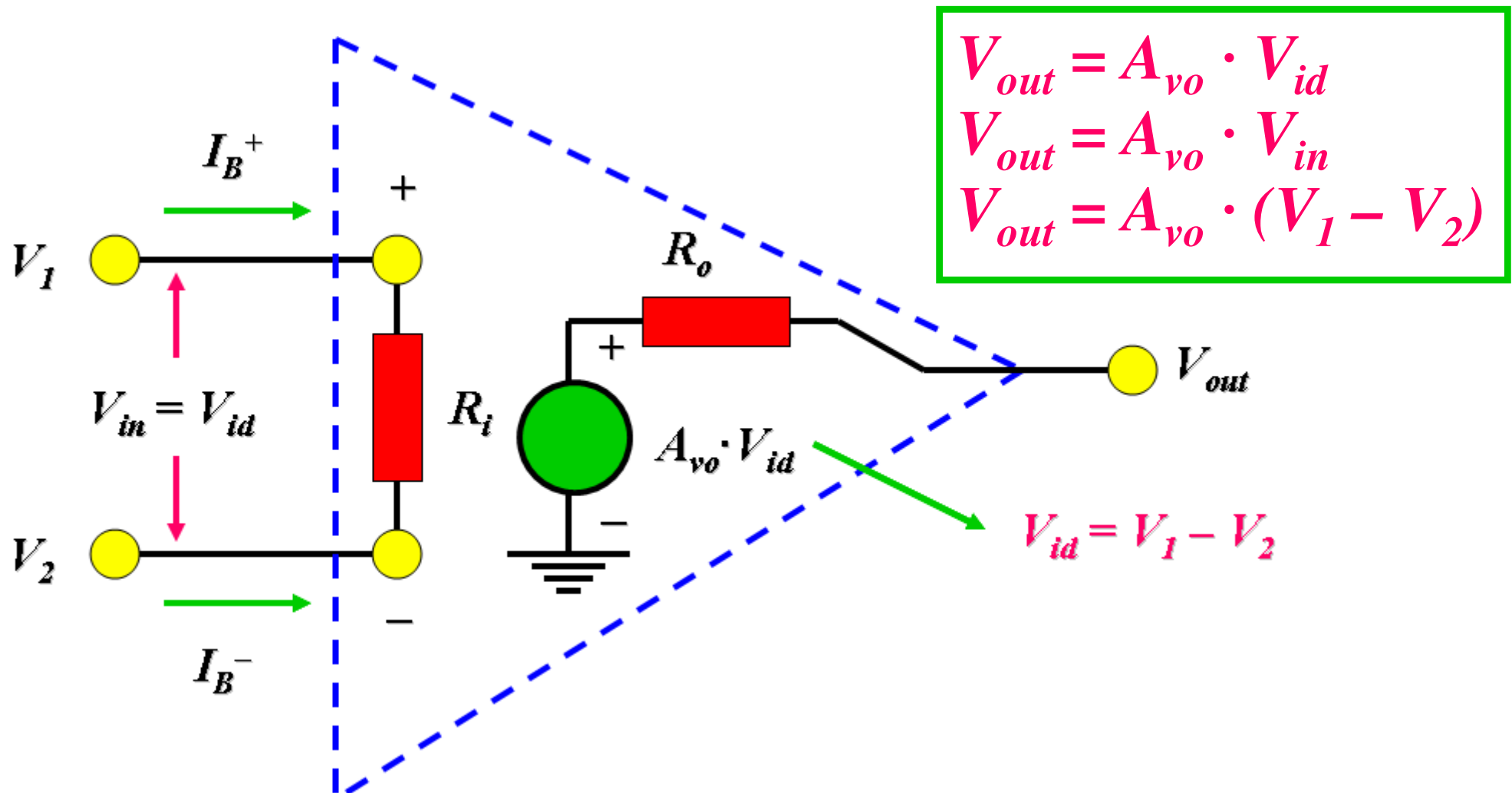
## Applications in Open Loop Configuration



# Practical Operational Amplifier
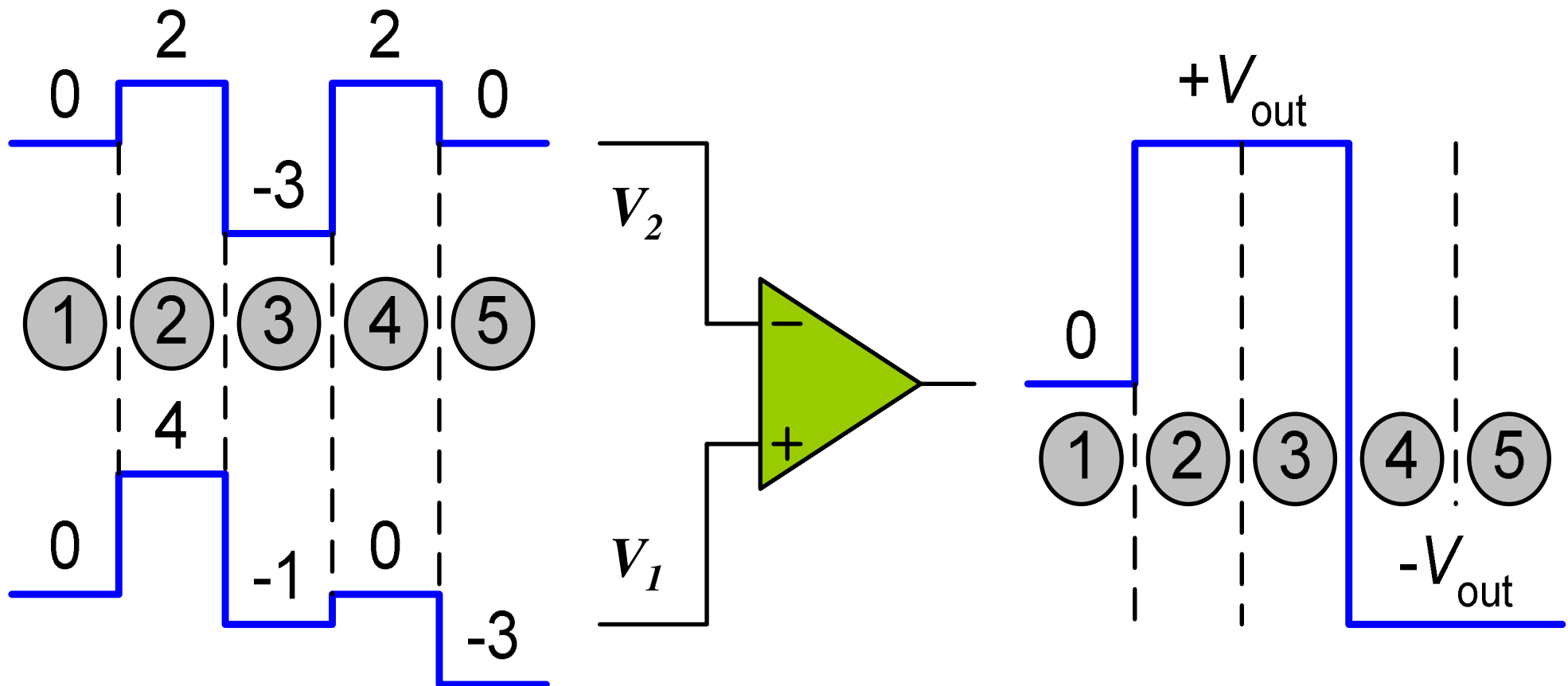
## Applications in Open Loop Configuration




# Open Loop Configuration

## 1. The Difference Amplifier
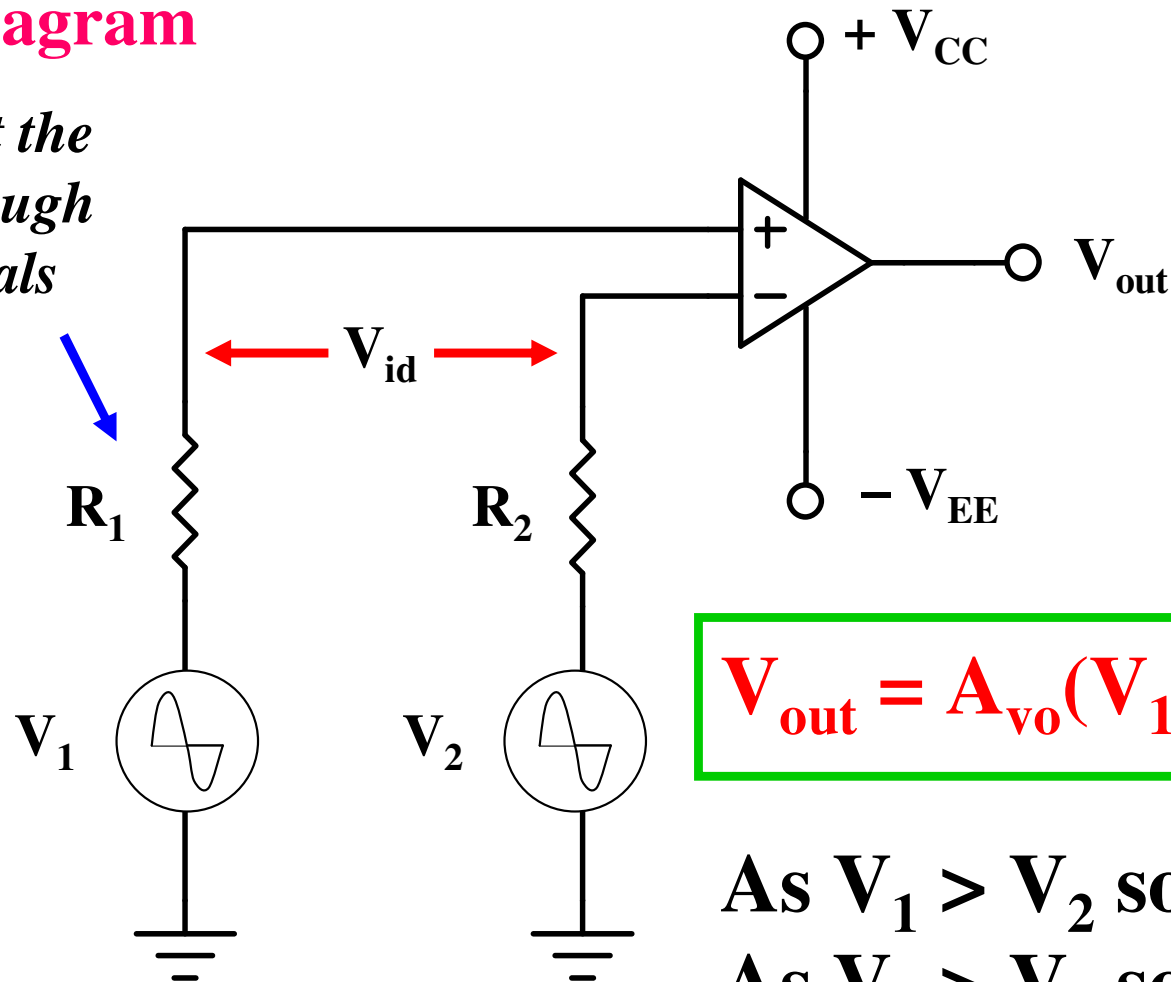
### Circuit Diagram

*used to limit the current through the terminals*



$$V_{out} = A_{vo}(V_1 - V_2)$$

As  $V_1 > V_2$  so  $V_{out} = +V_{sat}$



As  $V_2 > V_1$  so  $V_{out} = -V_{sat}$



# Open Loop Configuration

## 1. The Difference Amplifier


### Waveforms

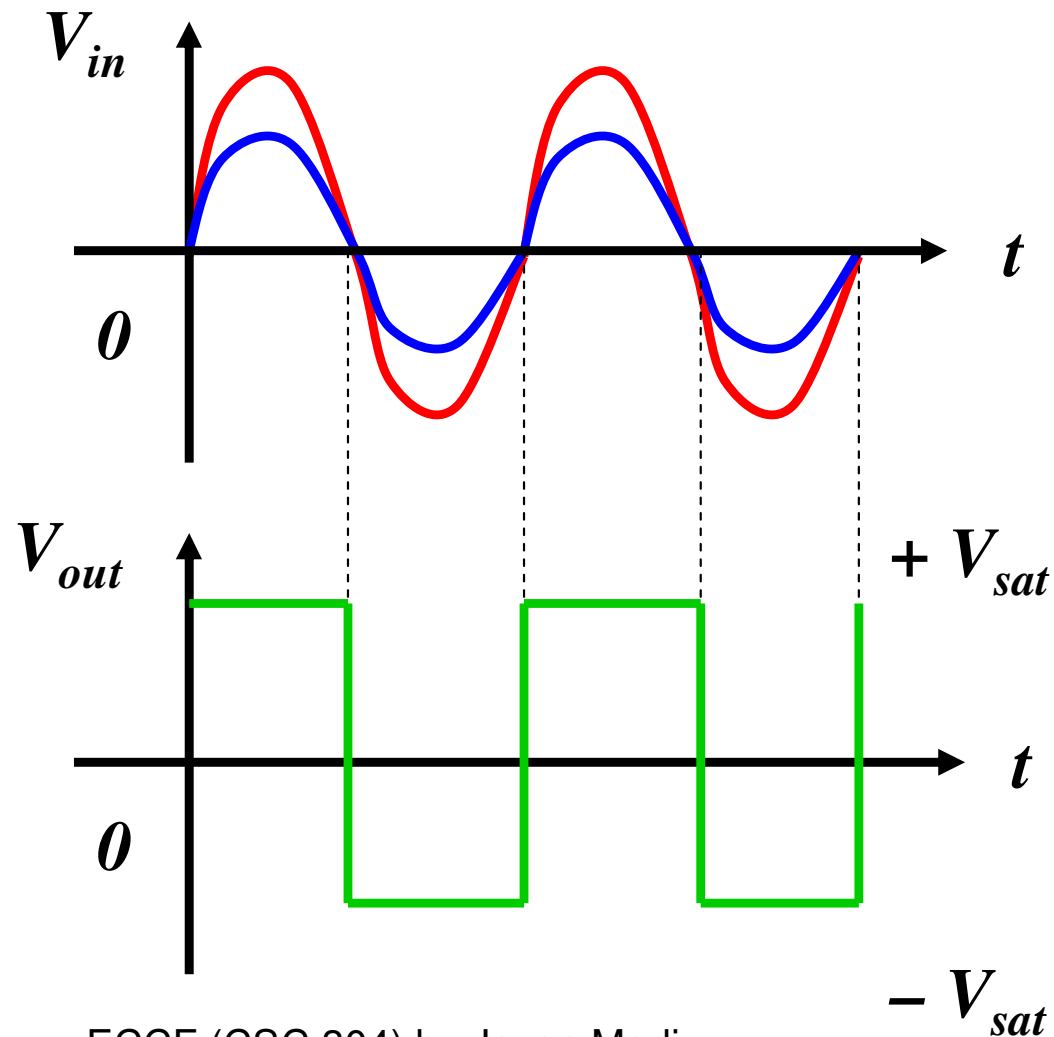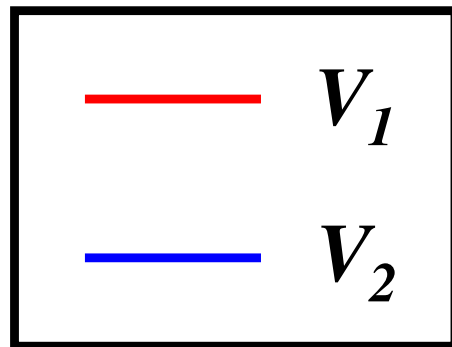

# Open Loop Configuration

## 2. The Inverting Amplifier

### Circuit Diagram

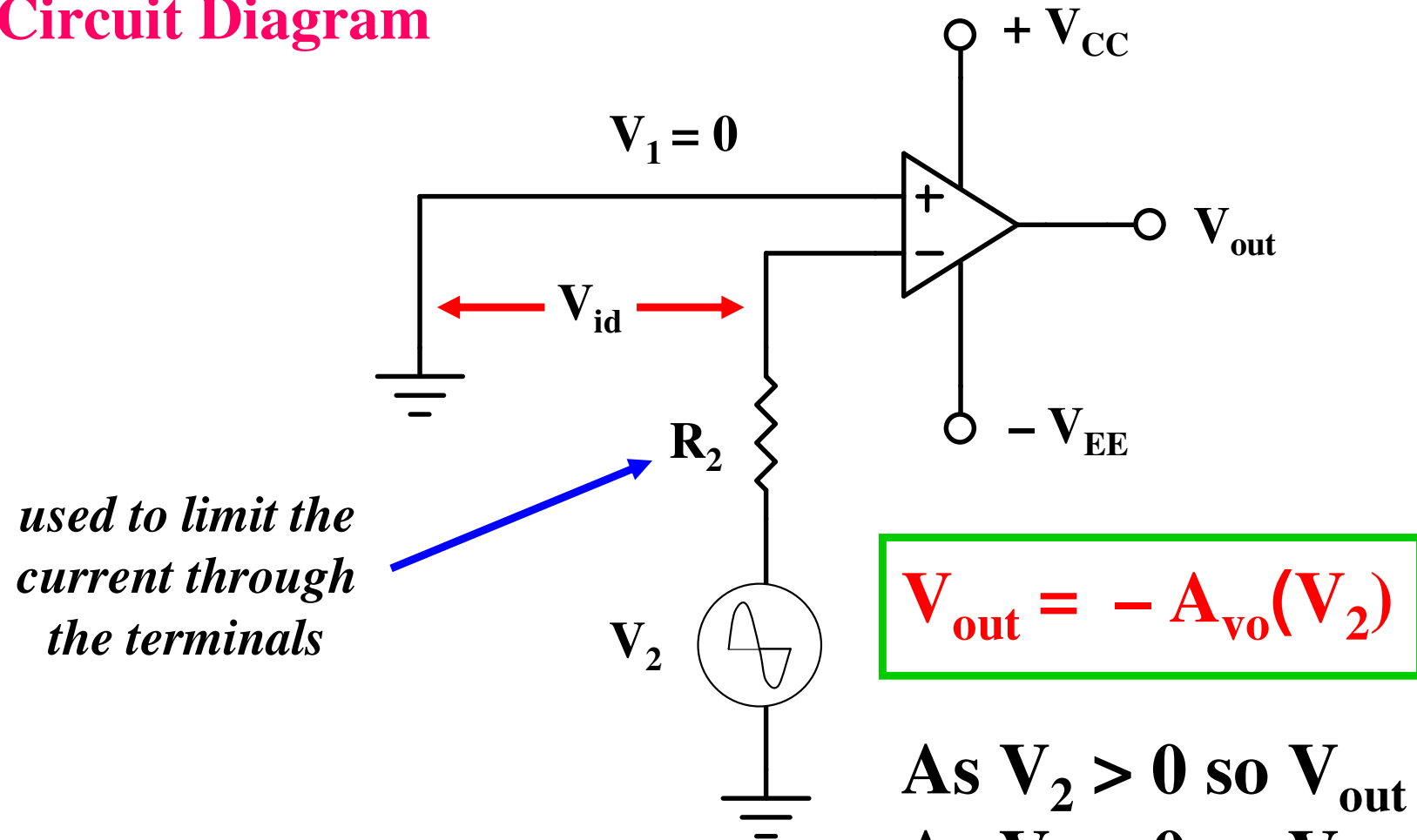

As  $V_2 > 0$  so  $V_{out} = -V_{sat}$


As  $V_2 < 0$  so  $V_{out} = +V_{sat}$

# Open Loop Configuration

## 2. The Inverting Amplifier
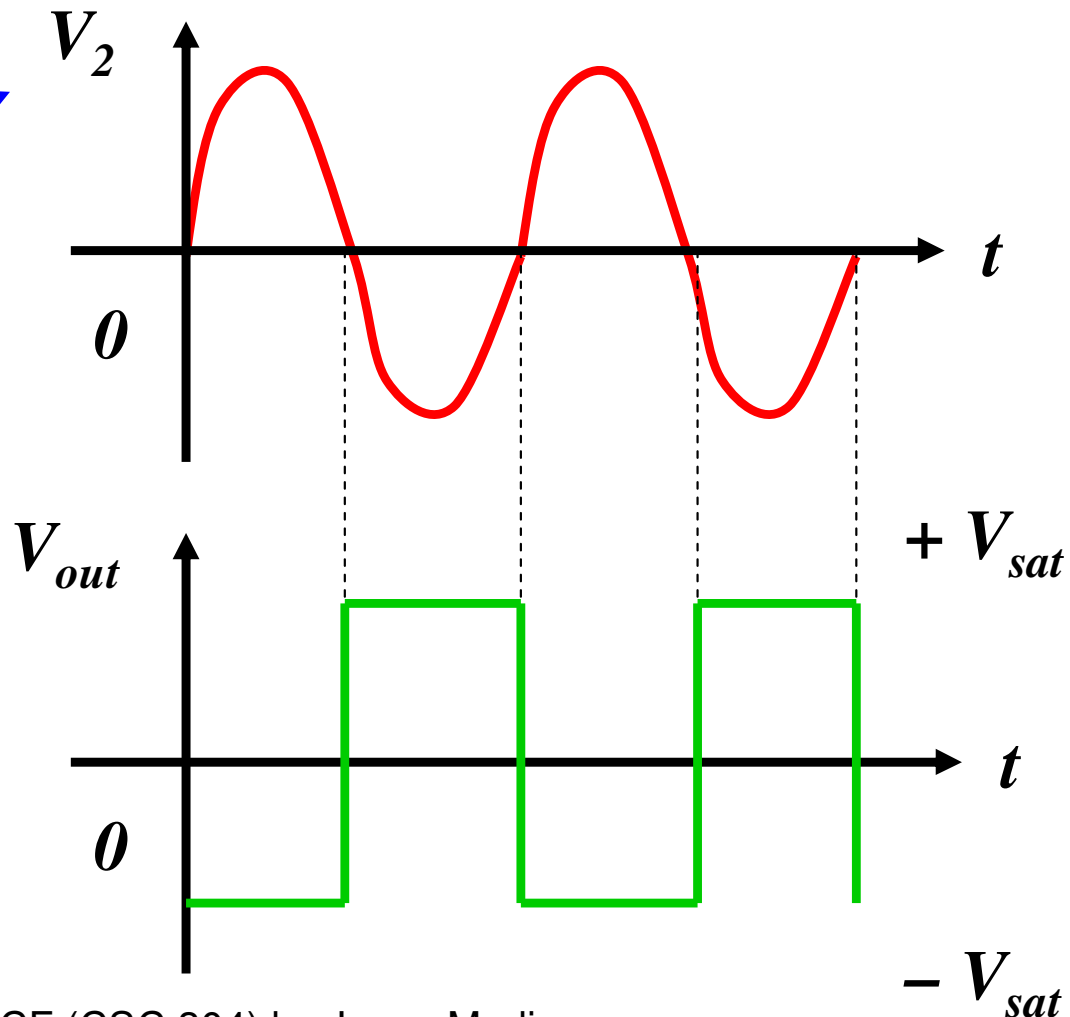
### Waveforms

*both input & output signals out of phase with each other*




# Open Loop Configuration

## 3. The Non – Inverting Amplifier
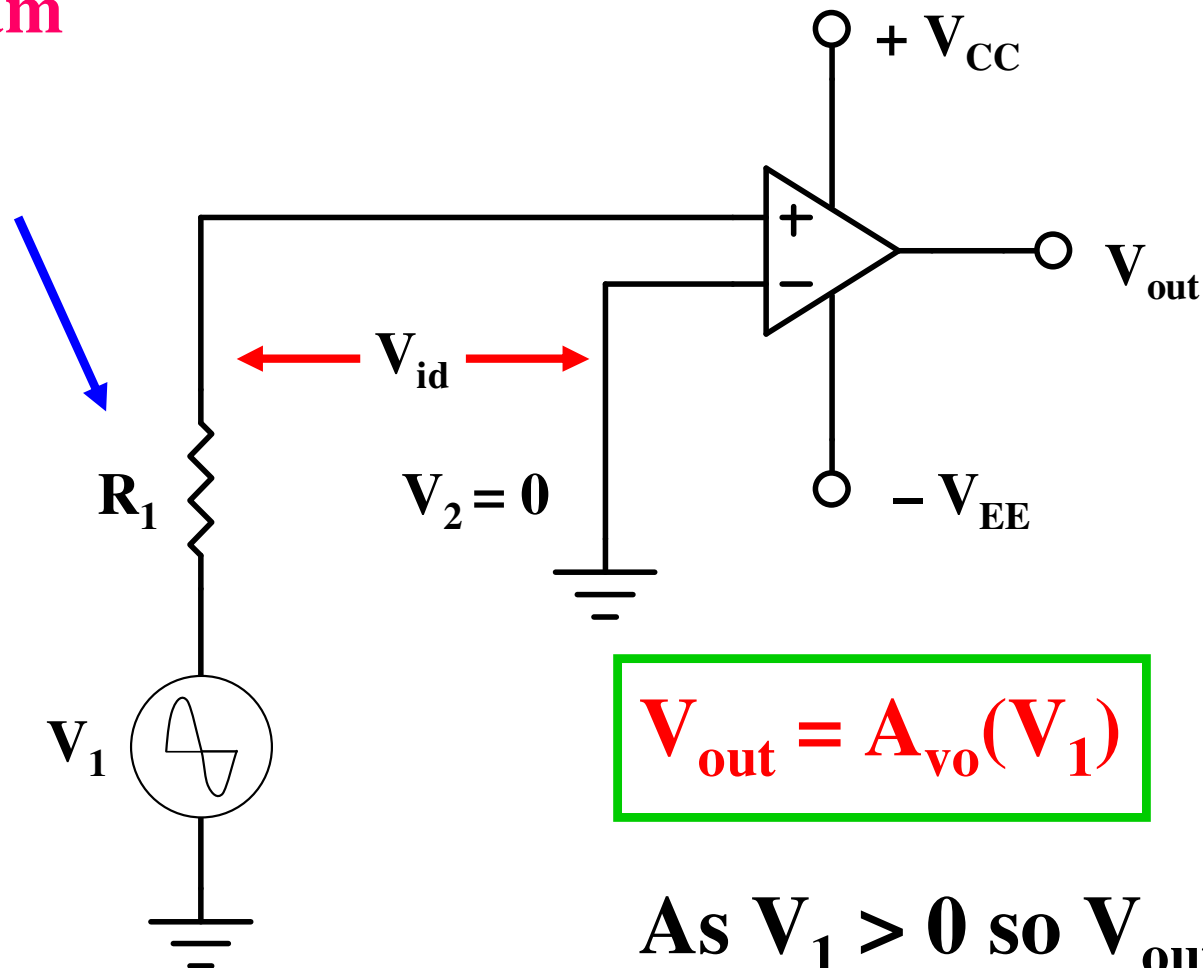
### Circuit Diagram

*used to limit the current through the terminals*



$$V_{out} = A_{vo}(V_1)$$

As  $V_1 > 0$  so  $V_{out} = +V_{sat}$


As  $V_1 < 0$  so  $V_{out} = -V_{sat}$

# Open Loop Configuration

## 3. The Non – Inverting Amplifier
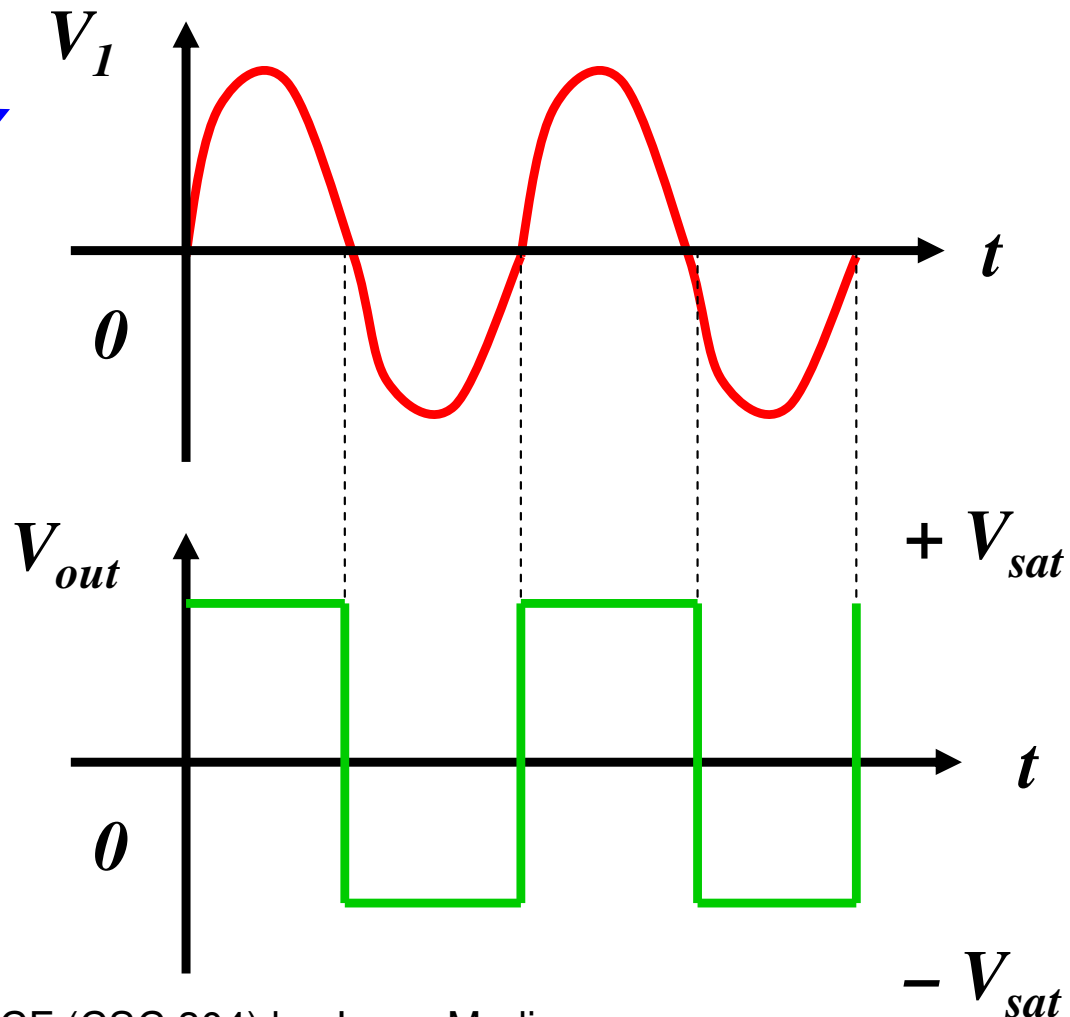
### Waveforms


*both input & output signals are in phase with each other*




# Open Loop Configuration

## Input Waveforms & Output Waveforms


*Difference Amplifier*

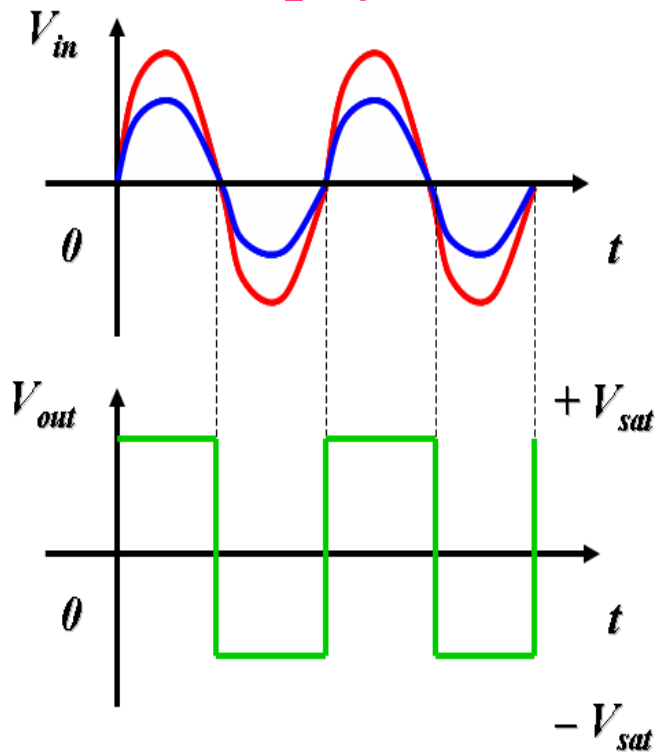

*Inverting Amplifier*

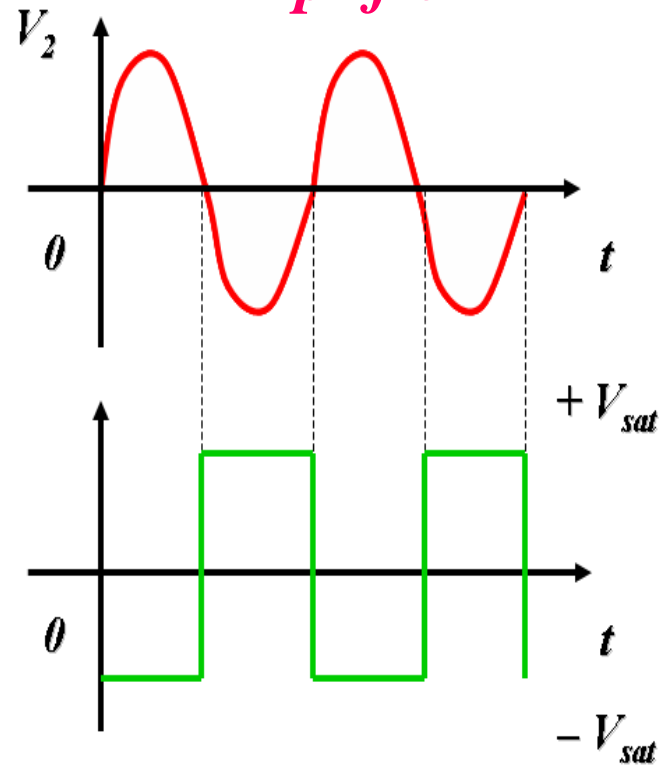


*Non – Inverting Amplifier*

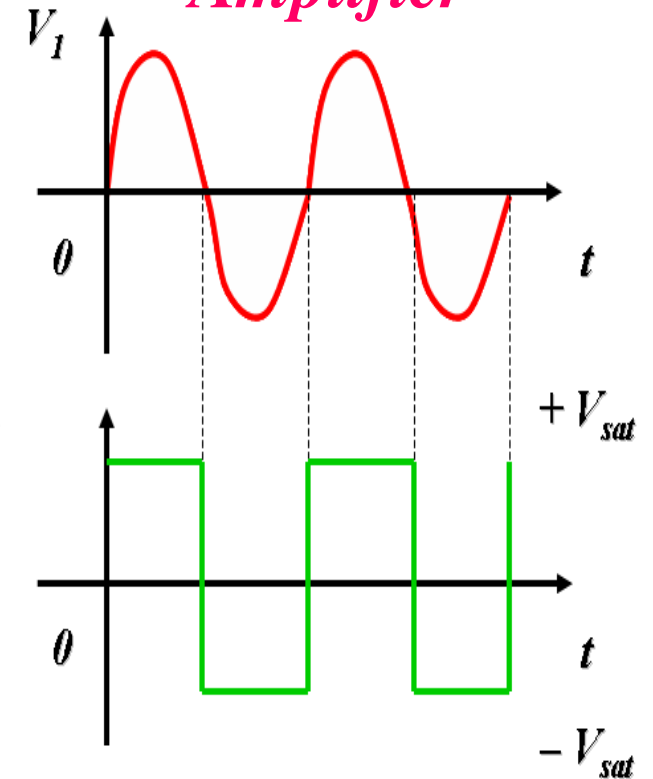

**WHERE'S THE AMPLIFICATION ???**

# Practical Operational Amplifier

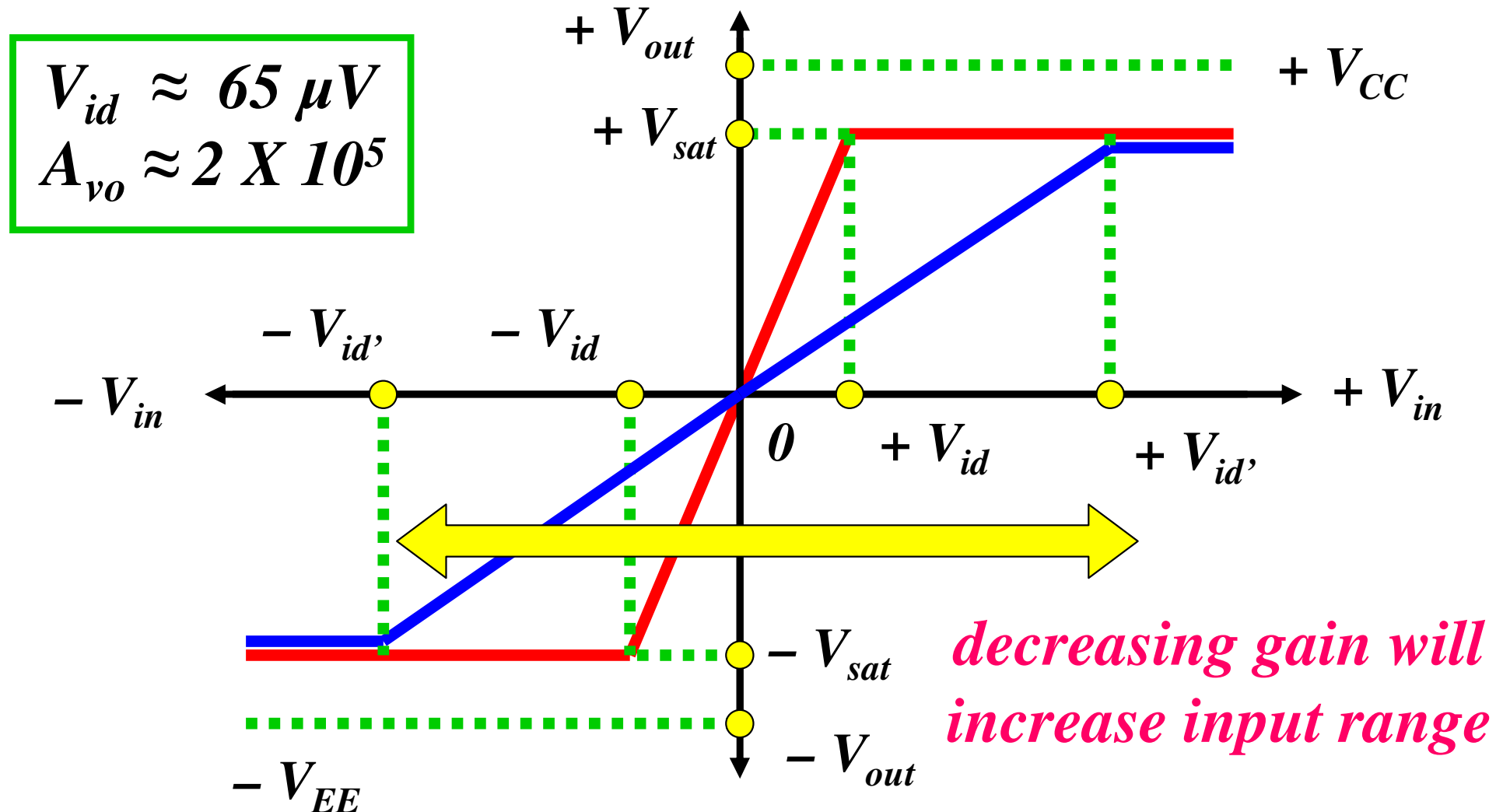
## ‘Manipulated’ Transfer Characteristics



# Practical Operational Amplifier

## Applications in Closed Loop Configuration


### Negative Feedback Connection

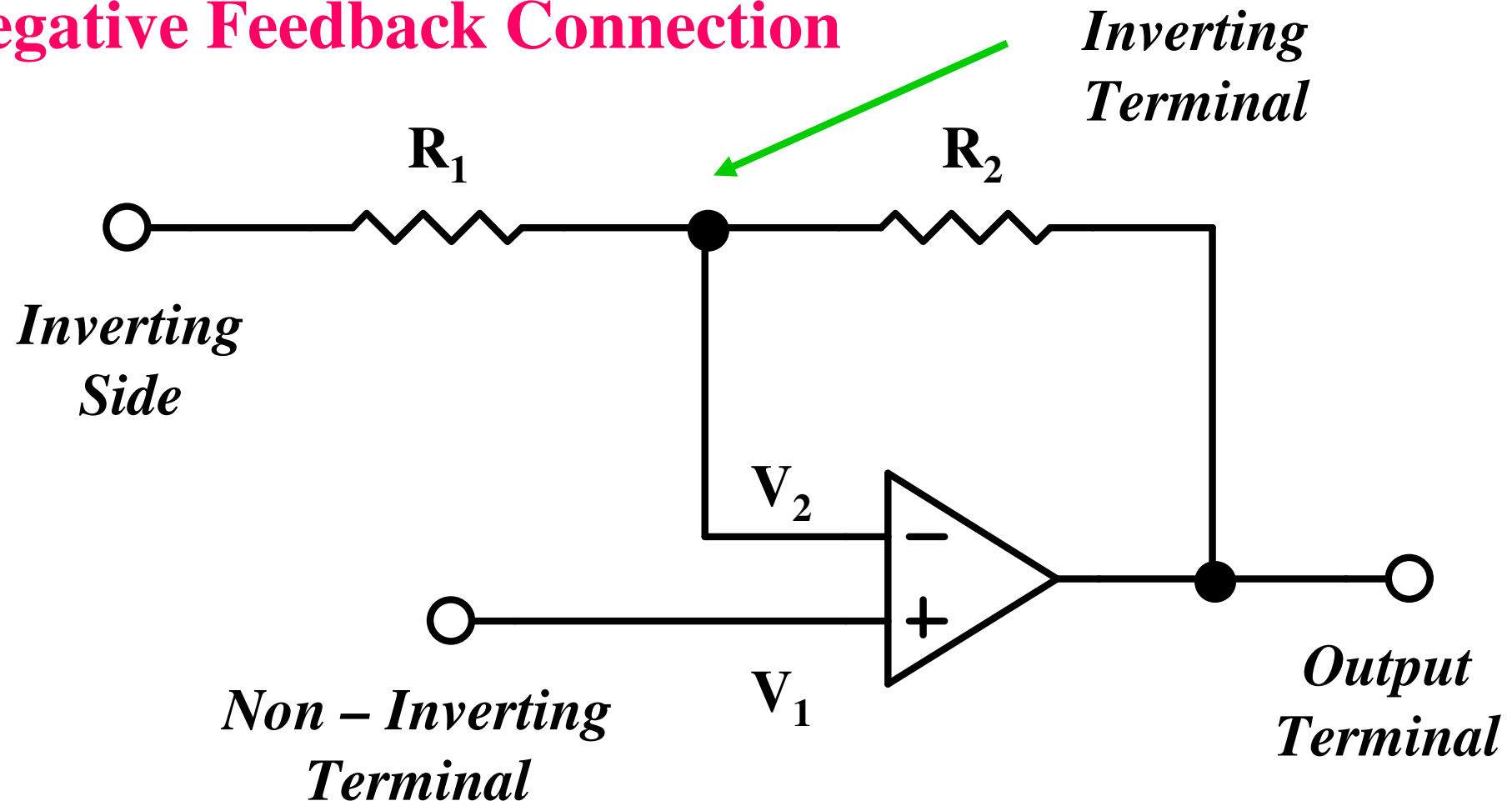




# Practical Op – Amp Analysis

## 1. Virtual Short Concept in Op – Amp

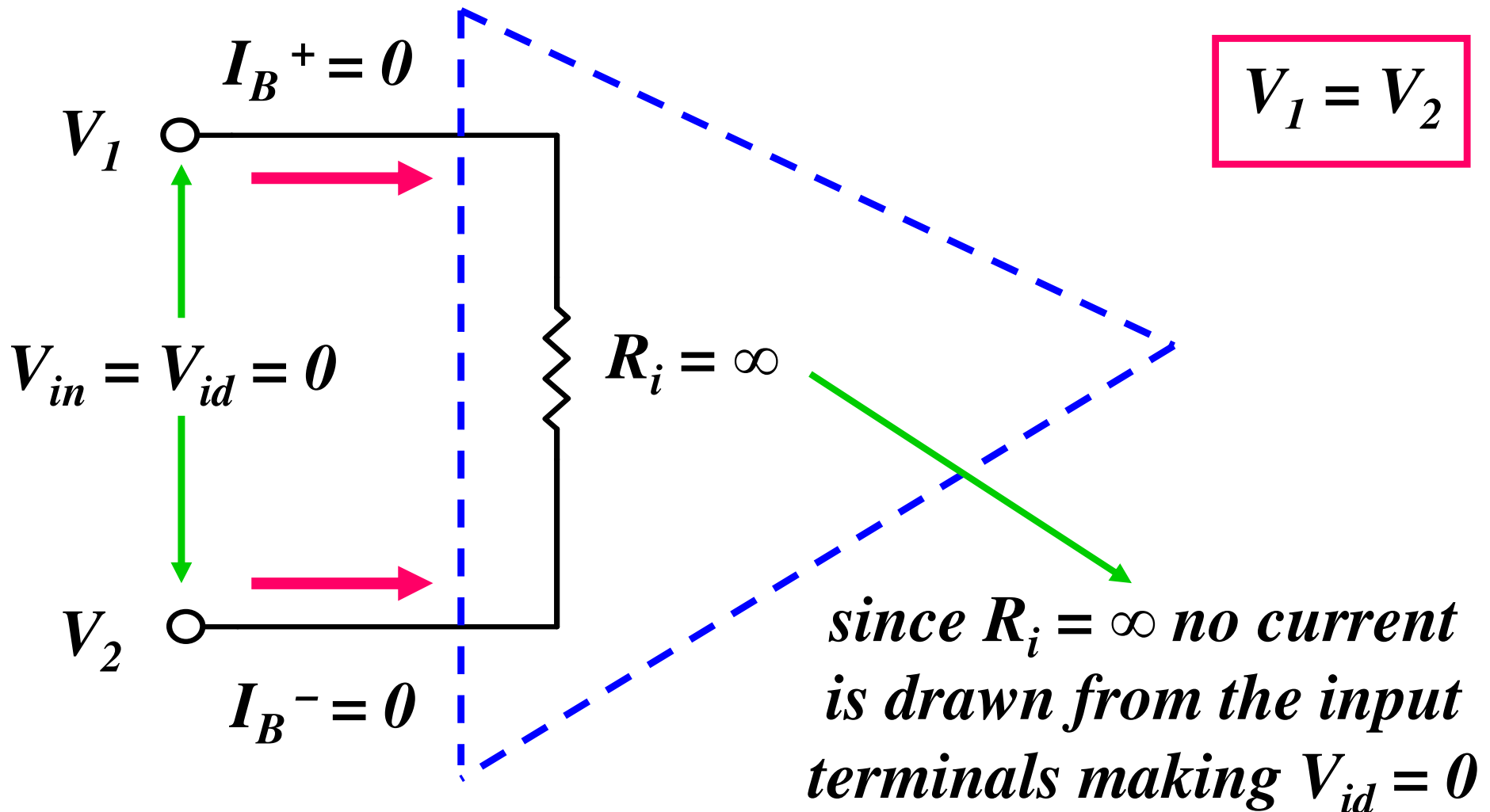

# Practical Op – Amp Analysis

## 2. Virtual Ground Concept in Op – Amp

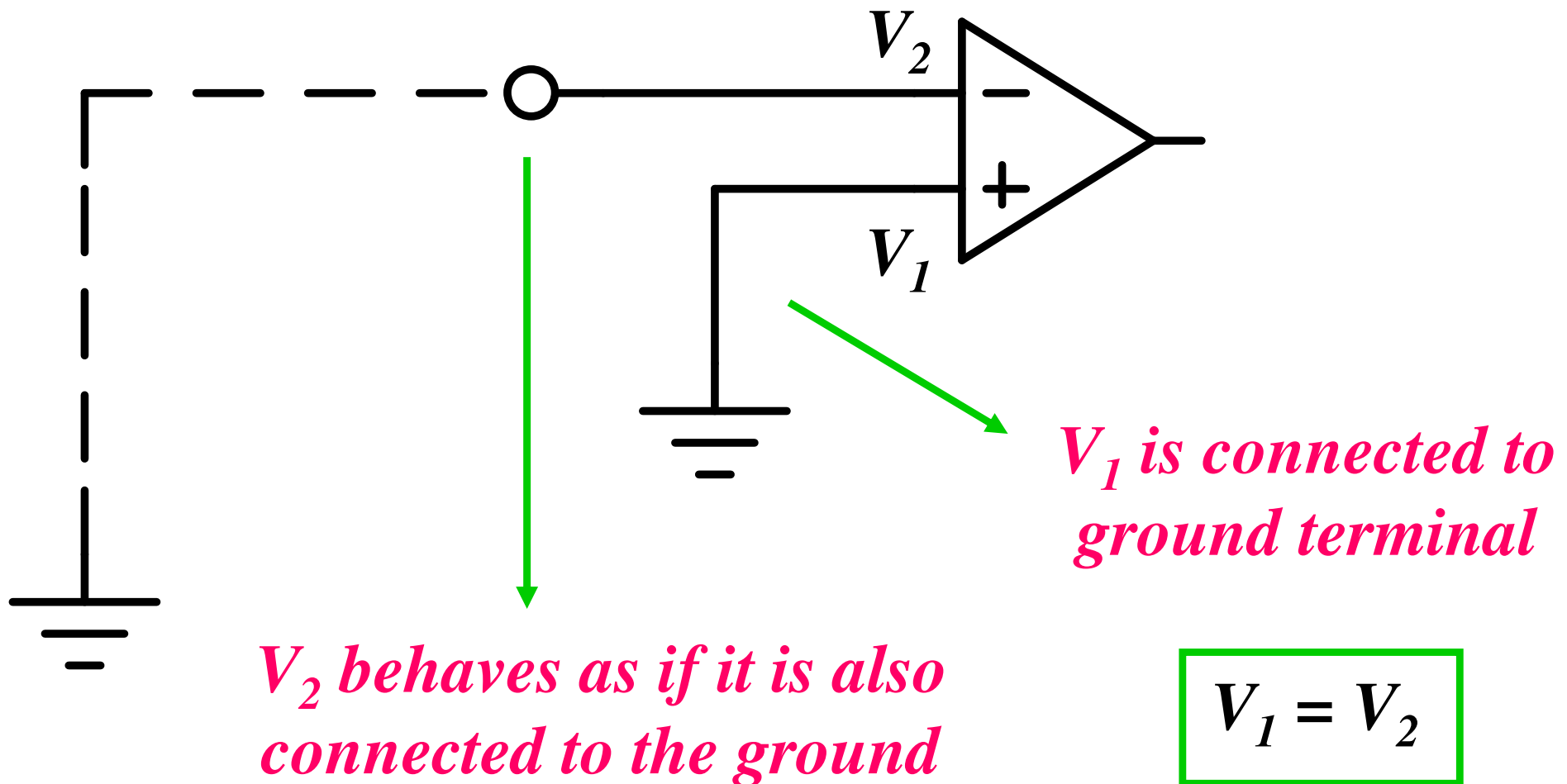

# Ideal Operational Amplifier

## Features of Ideal Operational Amplifier

- Open – loop voltage gain is **infinite**
- Input Impedance is **infinite**
- Output Impedance is **zero**
- Bandwidth is **infinite**
- CMRR is **infinite**
- Slew Rate is **infinite**
- Output Offset Voltage is **zero**
- Input Bias Currents are **zero**

*not possible  
to achieve in  
actual practice*

# Practical Operational Amplifier

## Features of Practical Operational Amplifier

- Large Open – Loop Voltage Gain ( $2 \times 10^5$ )
- Very high Input Impedance ( $2 \text{ M}\Omega$ )
- Very low Output Impedance ( $75 \Omega$ )
- Output Offset Voltage of upto  $\pm 15 \text{ mV}$
- High value of CMRR ( $80 \text{ dB} - 120 \text{ dB}$ )
- Small Bandwidth ( $5 \text{ Hz}$ )
- Finite Slew Rate ( $0.5 \text{ V}/\mu\text{s}$ )
- Input Bias Currents of upto  $500 \text{ nA}$

*features  
of  
 $\mu\text{A} 741$*

# D.C. Characteristics of Op – Amp


## 1. Input Bias Current ( $I_B$ )

- The input stage of op – amp is differential amplifier made up of either BJT or JFET
- These devices are biased in the active region of their operation by supplying some input current
- Ideally due to the extremely high input resistance of input stages, these currents are almost negligible
- Practically some of input current flows through both the op – amp input terminals

*These are called as the bias currents  $I_{B1}$  &  $I_{B2}$*

# D.C. Characteristics of Op – Amp

## 1. Input Bias Current ( $I_B$ )

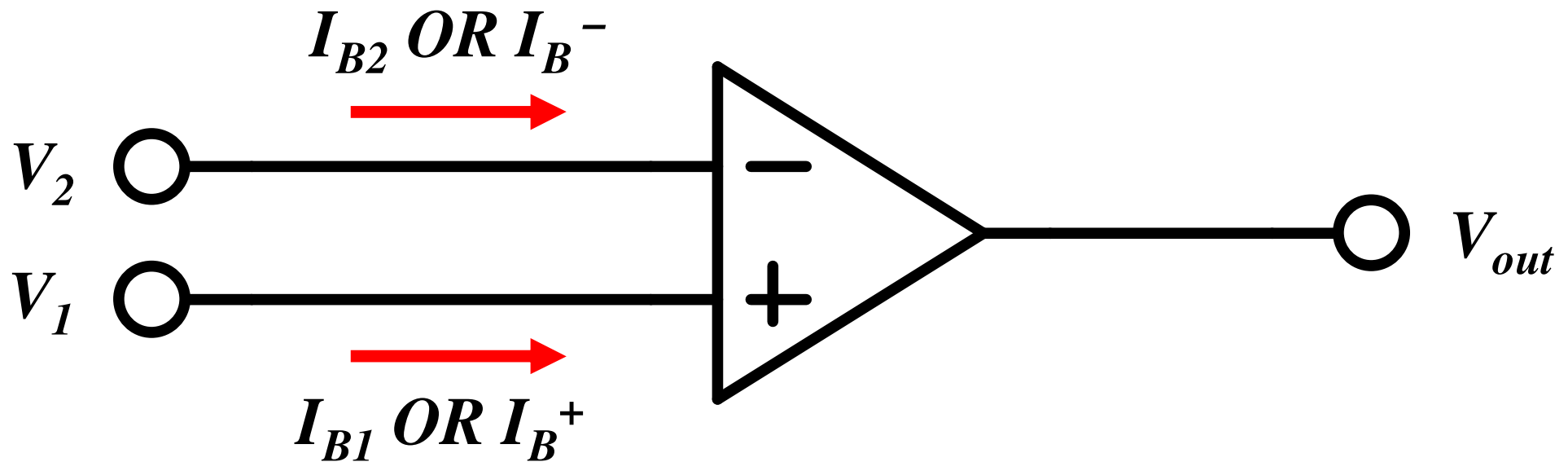


*average of the two currents entering op-amp terminals is called input bias current*

$$I_B = \frac{I_B^+ + I_B^-}{2}$$

# D.C. Characteristics of Op – Amp
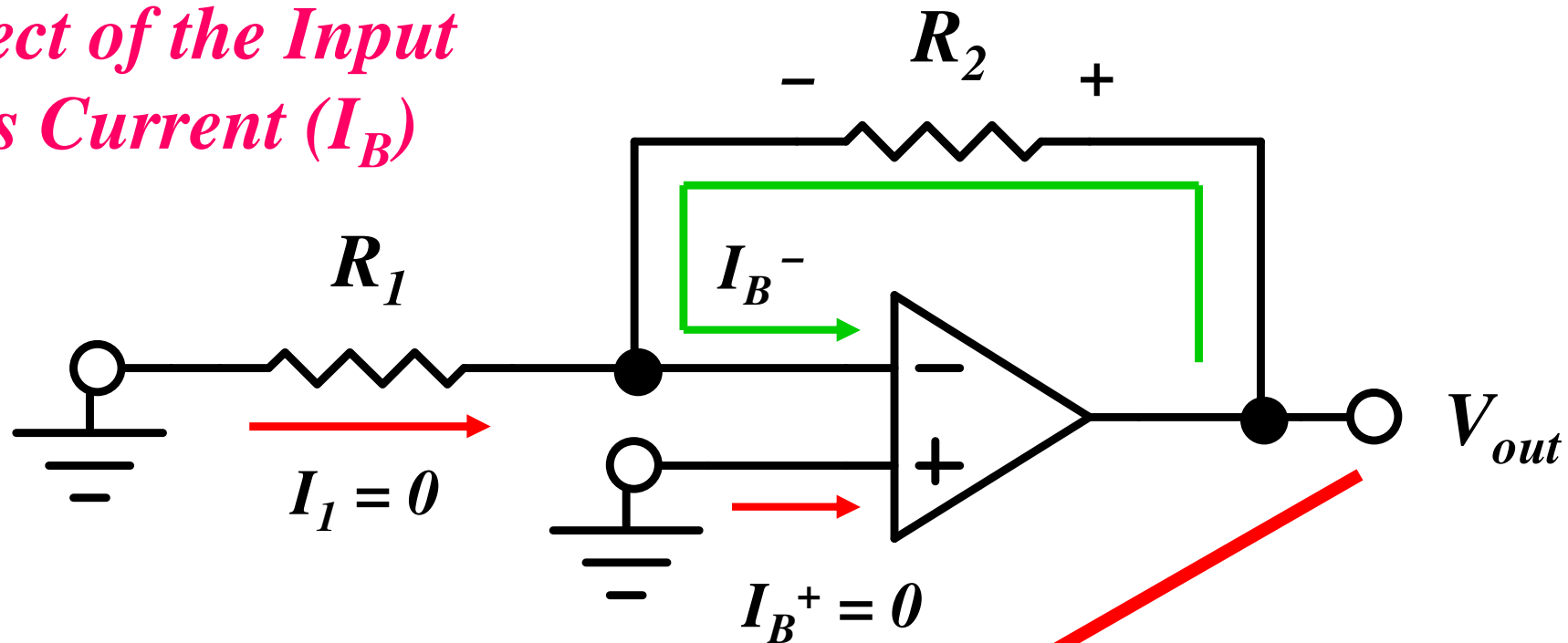
## 1. Input Bias Current ( $I_B$ )

*Effect of the Input Bias Current ( $I_B$ )*



$$V_{out} = (I_B^-)R_2$$

*presence of bias current results in an output offset*

*voltage  $V_{out} = V_{oos}$*

# D.C. Characteristics of Op – Amp

## 2. Input Offset Current ( $I_{ios}$ )

- Bias current compensation will work only if both bias currents are equal ( $I_B^+$  &  $I_B^-$ )
- Since input transistors can't be made identical there is some difference in the bias currents
- This small difference called as the input offset current ( $I_{ios}$ ) & is given by :-

$$|I_{ios}| = I_B^+ - I_B^-$$



# D.C. Characteristics of Op – Amp

## 3. Input Offset Voltage ( $V_{ios}$ )


- Shorting together the input terminals of the op – amp gives output voltage as  $V_{out} = 0$  since  $V_1 = V_2 = 0$
- Due to the mismatches between the two transistors of input stage of differential amplifier,  $V_{out} \neq 0$
- To force the output voltage ( $V_{out}$ ) to become zero, we need to apply some input voltage to the op – amp
- This is called as the input offset voltage ( $V_{ios}$ ) defined as amount to null the output voltage

*$V_{ios}$  is used for forcing to make  $V_{out} = 0$*

# D.C. Characteristics of Op – Amp
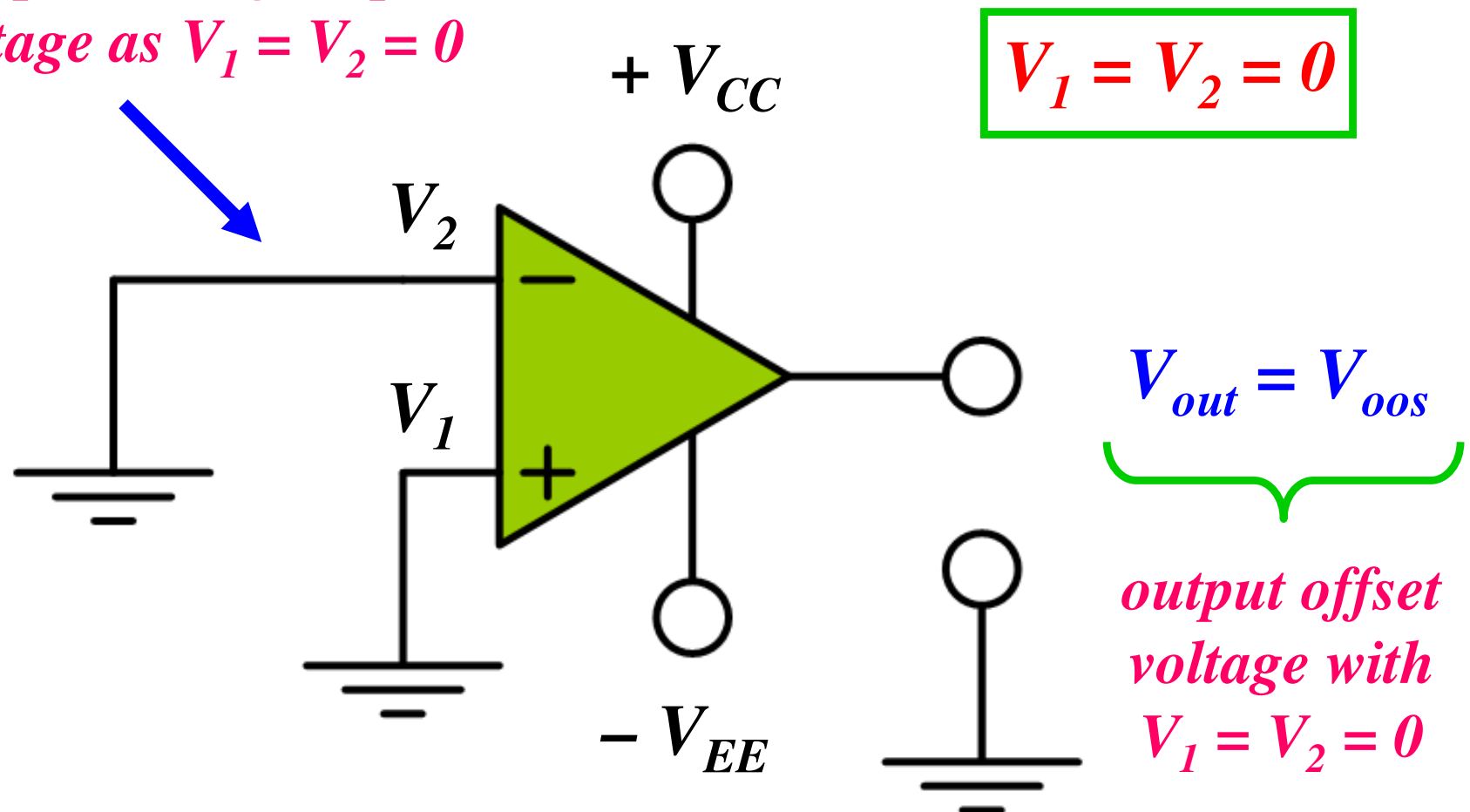
## 3. Input Offset Voltage ( $V_{ios}$ )


*Op – amp producing output offset voltage as  $V_1 = V_2 = 0$*



# D.C. Characteristics of Op – Amp
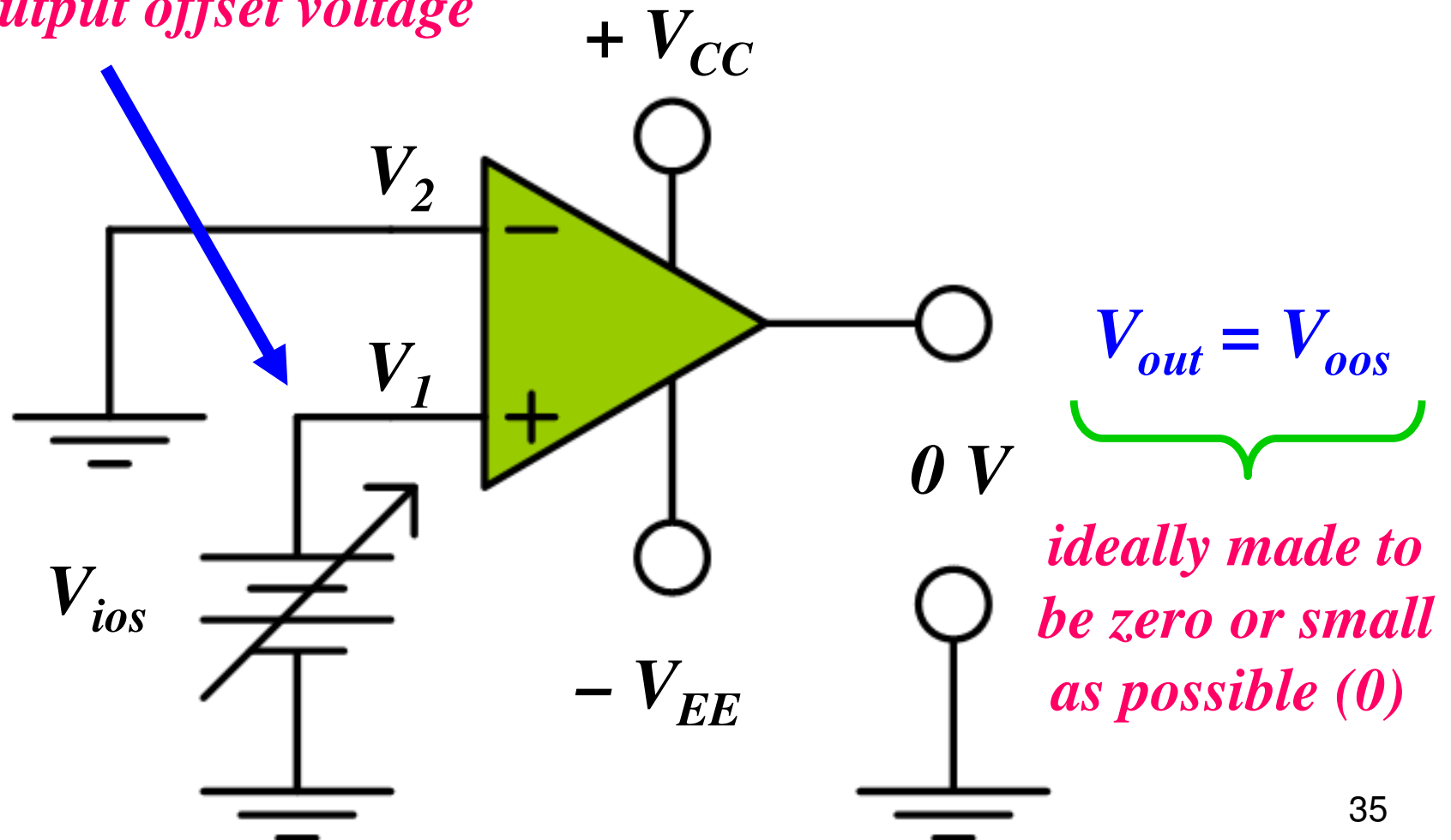
## 3. Input Offset Voltage ( $V_{ios}$ )

*Input offset voltage applied to null the output offset voltage*




*ideally made to be zero or small as possible (0)*

# D.C. Characteristics of Op – Amp
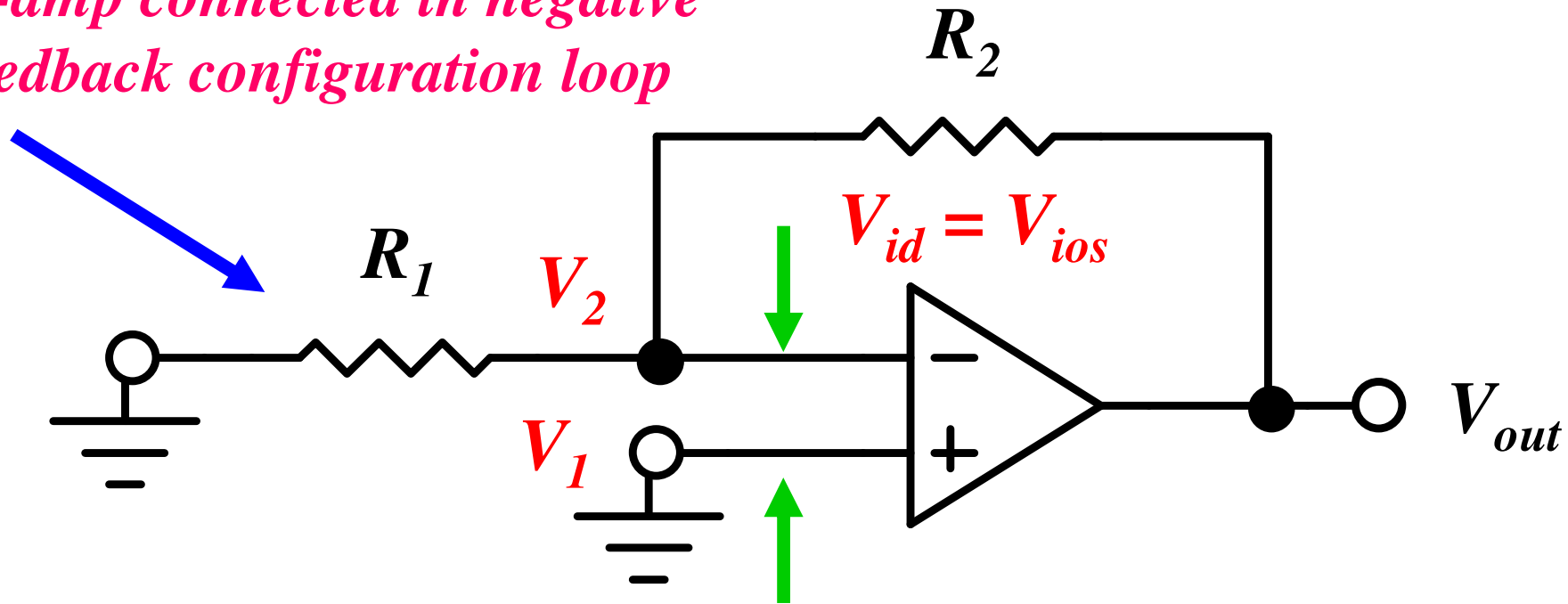
## 3. Input Offset Voltage ( $V_{ios}$ )


*Op-amp connected in negative feedback configuration loop*



*due to unequal bias currents as  $I_{B1} \neq I_{B2}$  there exists voltages hence potential difference between  $V_1$  &  $V_2$*

# D.C. Characteristics of Op – Amp

## 3. Input Offset Voltage ( $V_{ios}$ )

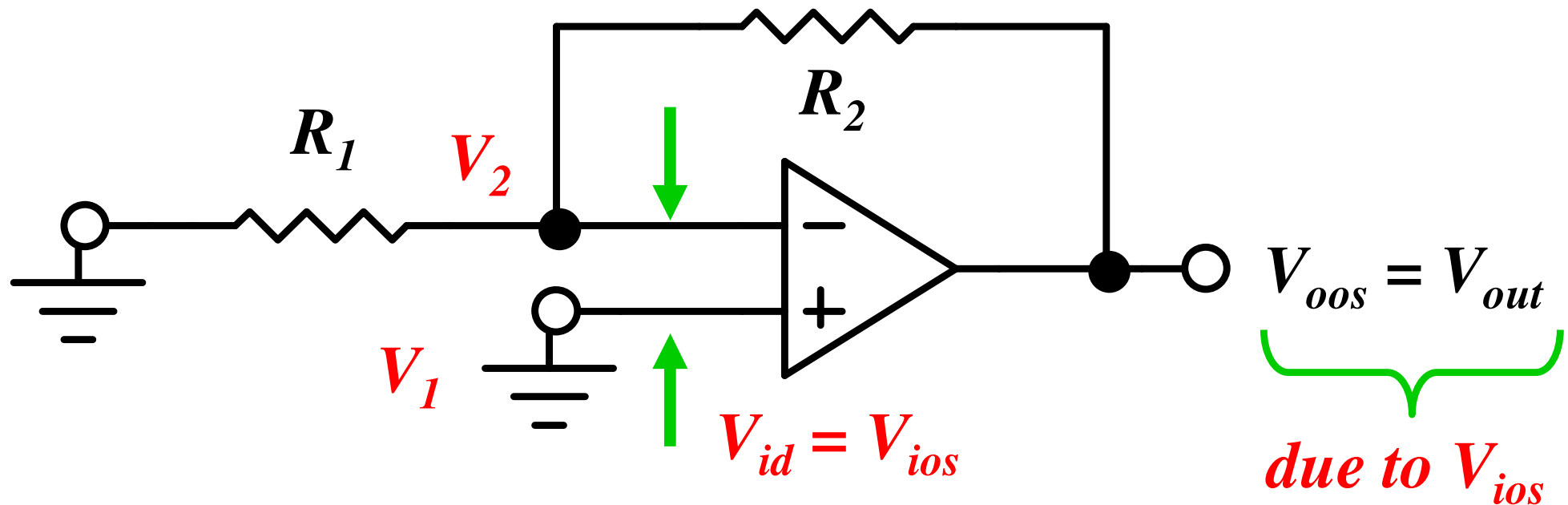

$$V_{out} = V_{oos} = \left( 1 + \frac{R_2}{R_1} \right) V_{ios}$$

*measuring the  $V_{oos}$   
helps to calculate  
the input offset  $V_{ios}$*

# D.C. Characteristics of Op – Amp

## 4. Output Offset Voltage ( $V_{oos}$ )

- Output offset voltage is the voltage at output terminal of the op – amp without any input applied to it
- Output offset voltage results due to the effect of input bias current current ( $I_{B2}$ ) which can be minimized
- By compensating resistor ( $R_{comp}$ ) it can be minimized but effect remains due to input offset current ( $I_{ios}$ )
- It is due to the input offset voltage ( $V_{ios}$ ) resulting at the op-amp input terminals without any input

$$V_{oos} = f(I_{B2}, I_{ios} \& V_{ios})$$

# Input Offset Voltage Compensation

## (a) Op – Amp with offset null terminals


- Many op-amps, including the IC 741C have a pair of external offset null pins as shown in the figure
- 10 k $\Omega$  potentiometer is connected between the offset null pins 1 & 5 with wiper connected to  $-V_{EE}$
- The potentiometer is gradually adjusted around the voltage of  $-V_{EE}$  for zero output voltage (minimum)
- This procedure has to be repeated many times using an op-amp for practical applications

*Refer class note book for circuit diagram*

# Input Offset Voltage Compensation
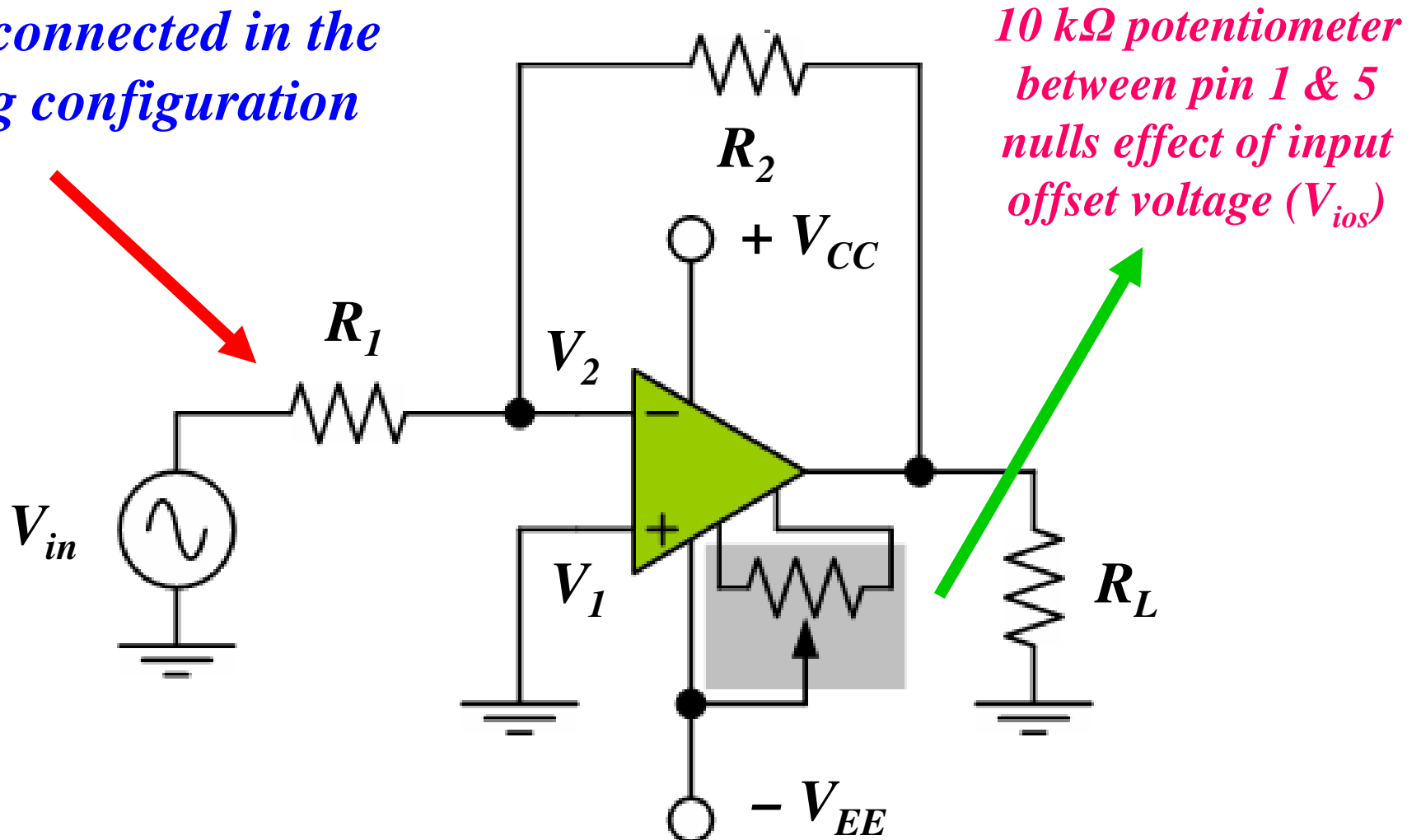
## (a) Op – Amp with offset null terminals

*Op-amp connected in the inverting configuration*





# Op – Amp Transient Analysis


## (b) Slew Rate (SR) Characteristics

- Slew Rate (SR) is defined as maximum rate of change of op – amp output voltage with time
- Higher the value of the slew rate, better is the op – amp since  $V_{out}$  can change as fast as  $V_{in}$

$$SR = \left. \frac{dV_{out}}{dt} \right|_{max}$$

# Slew Rate (SR) Characteristics
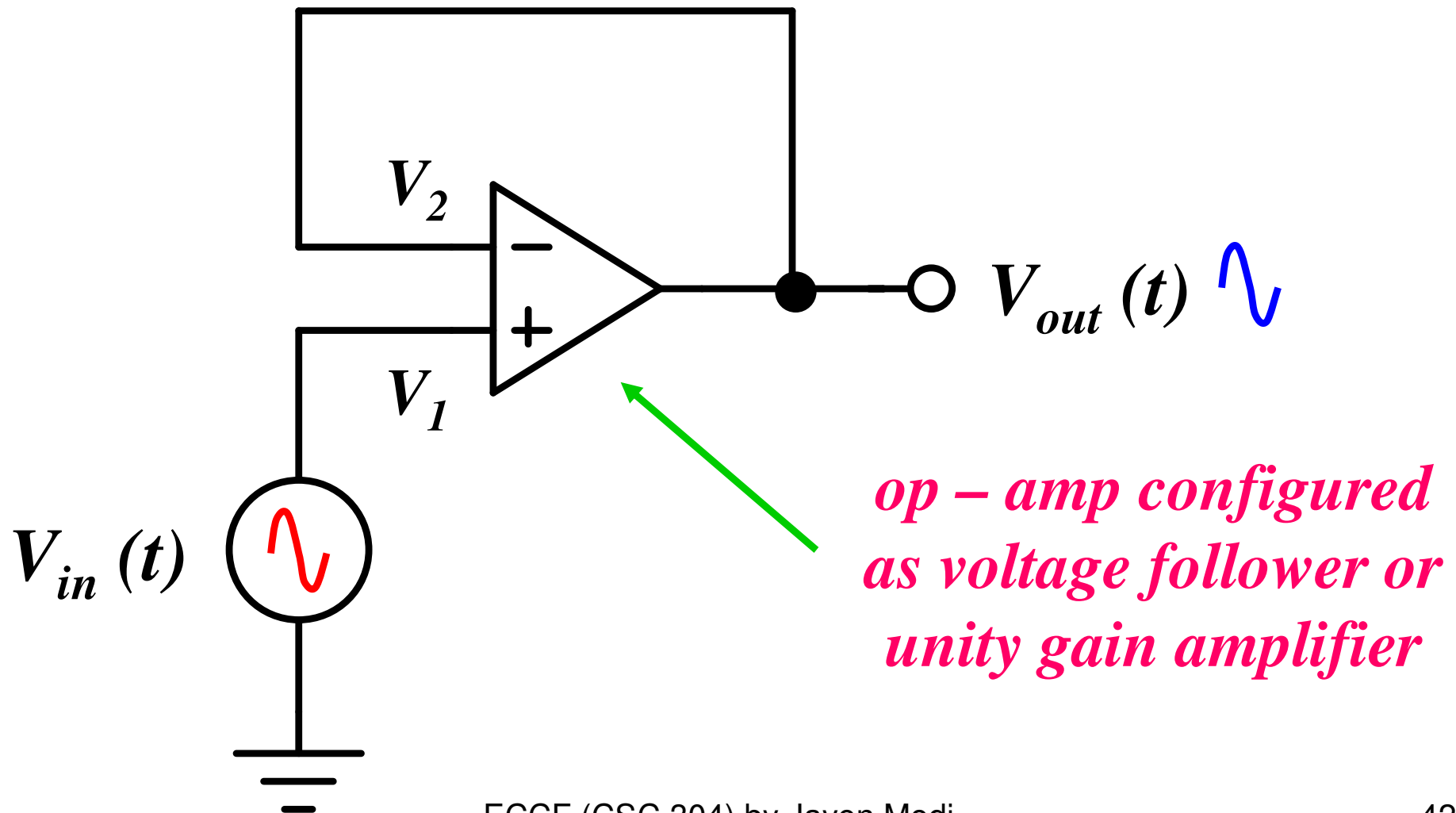
## Circuit Diagram of Unity Gain Amplifier



# Slew Rate (SR) Characteristics

## Mathematical Analysis & Derivations

*Given  $V_{in}(t) = V_m \sin \omega_m t$   
hence  $V_{out}(t) = V_m \sin \omega_m t$*  } *since op – amp configured  
as voltage follower (buffer)*

*Differentiate  $V_{out}(t)$  with respect to time :-*

$$\frac{dV_{out}}{dt} = V_m \cdot \omega_m \cdot \cos \omega_m t$$

*now maximize  $dV_{out} / dt$  by  
putting term  $\cos \omega_m t = 1$*

$$\left. \frac{dV_{out}}{dt} \right|_{max} = V_m \cdot \omega_m \quad \longrightarrow \quad SR = \left. \frac{dV_{out}}{dt} \right|_{max}$$

$$\text{hence } SR = V_m \cdot 2\pi f_m \text{ where } \omega_m = 2\pi f_m$$

# Slew Rate (SR) Characteristics

## Limits on Voltage ( $V_m$ ) & Frequency ( $f_m$ )

$$\text{Slew Rate (SR)} = 2 \pi f_m V_m$$

*please refer your class notebook for equation*

$$f_m (\text{max}) = \frac{SR}{2 \pi V_m}$$

$$V_m (\text{max}) = \frac{SR}{2 \pi f_m}$$

*maximum values of the amplitude & frequency for the given slew rate*